

**IES / GATE**

---

**Electrical Engineering**

**VOLUME-VI**

**Electrical Machines**



# Contents

**Electrical Machines**


**1-348**



## Electrical Machines

Capable of Continuous Electromechanical Conversion is called Electrical machines.

### Transformers

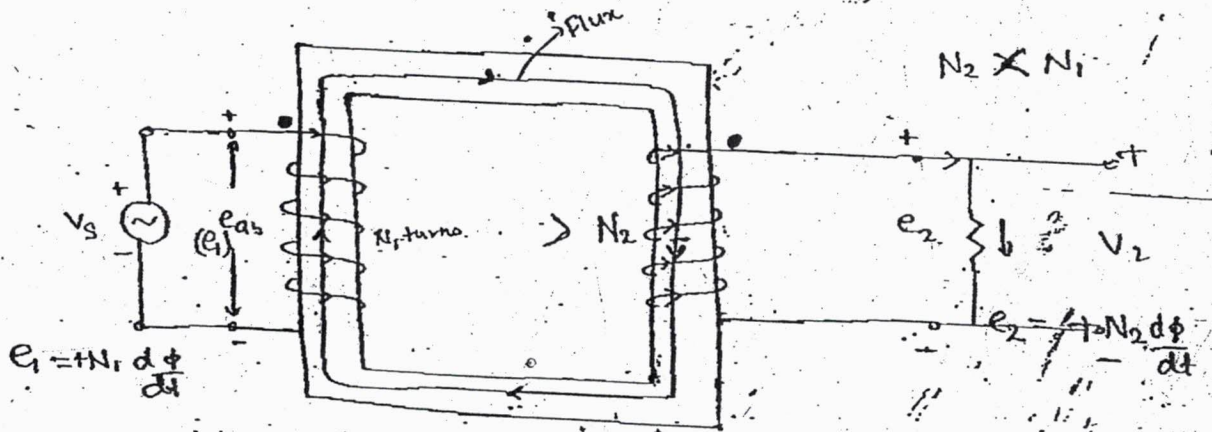

Core: - provide low reluctance magnetic path.


\* According to Lenz's law, the direction of induced emf is such that if it is allowed to cause a current by short circuiting the coil then the current so produced opposes the causes.

Thus, 
$$e = \pm \frac{d\lambda}{dt}$$


$$e_{ab} = + N_1 \frac{d\Phi}{dt}$$

when  $\lambda = \text{flux linkage} = N\Phi$ .

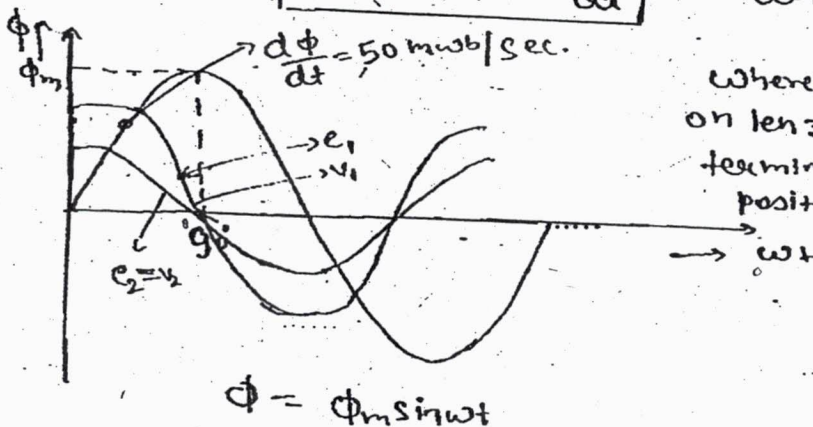where the sign depends on Lenz's law and which terminal is taken as positive.




ω also denoted

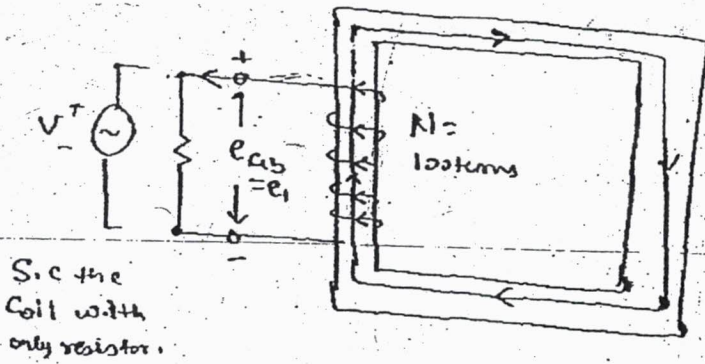

$$e_1 = e_{ab} = N_1 \frac{d\phi}{dt}$$

$$= 100 \times 50 \times 10^{-3}$$

$$= 5 \text{ volt}$$

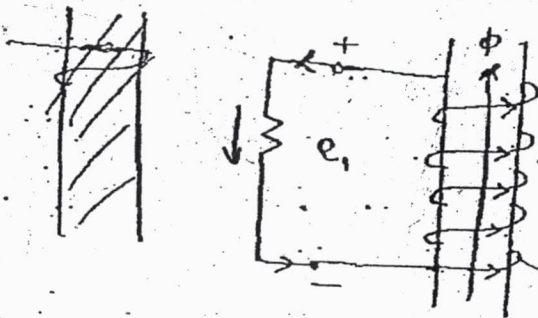

$$e_1 = -N_1 \frac{d\phi}{dt}$$

$$= -100 \times 50 \times 10^{-3}$$

$$= -5 \text{ V}$$

Sense of eddy changes

$$e_1 = N_1 \frac{d\phi}{dt}$$

$$= N_1 \frac{d}{dt} (\phi_m \sin \omega t)$$

$$= N_1 \phi_m \omega \cos \omega t$$

$$= N_1 \phi_m \omega \sin(\omega t + 90^\circ)$$

$$E_1 = \frac{N_1 \phi_m \omega}{\sqrt{2}}$$

$$E_1 = \sqrt{2} \pi f \phi_m N_1$$

Induced Emf equation



Concept of phasors

$$\sum v = 0$$

$$-e_1 + v_1 = 0$$

$$\Rightarrow v_1 = e_1$$

$$\Rightarrow \vec{E}_1 = \vec{V}_1$$

$$\vec{E}_1 = \vec{V}_1$$

$$\vec{V}_2 = \vec{E}_2$$

Phasor diagram of ideal X-former on no-load

Vector has a fixed magnitude & fixed direction.

But Sinusoids are the phasors not the vectors.

Phasor diagrams only shows phase relation.

$\vec{E}_1 = \vec{V}_1$  it does not mean  $\vec{E}_1$  supports  $\vec{V}_1$

but in vector,

$\vec{A}$  (concept of vector)


$$\vec{A} + \vec{B} = 0 \text{ (they are opposing)}$$

but in phasor, it is not determined.

Concept of phasors


- A phasor diagram has no meaning without ckt diagram and vice-versa.
- Phasor diagram only show that both  $\vec{E}$  &  $\vec{V}$  are rising together or decaying together and lag & lead and nothing else.
- They are supporting and opposing each other is determined by circuit diagram.

Sense of winding is changed here.

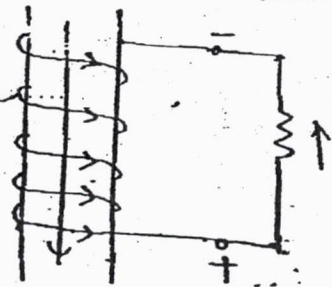
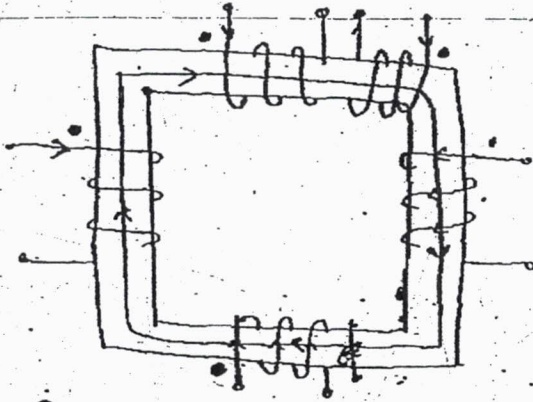
## Dot Convention

If the currents enters or leaves through the dot simultaneously, then the fluxes are additive.



Only the first dot is assigned. The remaining dots follow automatically depending upon the sense of winding.

As applied to transformer, therefore if the current enters through the dot in one winding then it should leave through the dot from the other winding to satisfy lenz law. In other words the dots have the same instantaneous polarity.

$$e_2 = +N_2 \frac{d}{dt} (\Phi_m \sin \omega t)$$

$$= +N_2 \Phi_m \omega \cos \omega t$$

$$= N_2 \Phi_m \omega \sin(\omega t + 90^\circ)$$

$$\Rightarrow E_2 = \frac{N_2 \Phi_m \omega}{\sqrt{2}}$$

$$E_2 = \sqrt{2} \pi f \Phi_m N_2$$



Ideal transformer

- 1) No losses
- 2) Infinite permeability

$$\Phi = \frac{NI}{S \text{ -reluctance}}$$

$$\Rightarrow NI = \Phi S = \Phi \frac{l}{\mu A} \Rightarrow NI = \Phi \times \frac{l}{\mu \times A}$$

- No winding losses
  - No core losses
  - No exciting current required
  - Zero magnetizing current.
- $= 0$  though  $\Phi \neq 0$

Property of a magnetic ckt.

If any magnetic ckt. is applied with an alternating excitation then it must produce an emf. which is equal and opposite in nature.

MMF balance of ideal X-former:-

$$N_1 \bar{I}_1 = N_2 \bar{I}_2 = 0$$

$$N_1 \bar{I}_1 = N_2 \bar{I}_2$$


$$\Rightarrow \bar{I}_1 = \frac{N_2}{N_1} \times \bar{I}_2 = \frac{I_2}{a} = \bar{I}_2'$$

Primary current referred to secondary

$$\frac{V_1}{V_2} = \frac{E_2}{E_1} = \frac{N_1}{N_2} = \frac{1}{a} = \frac{I_2}{I_1} = \frac{I_2^*}{I_1^*}$$


Turns ratio or Voltage ratio
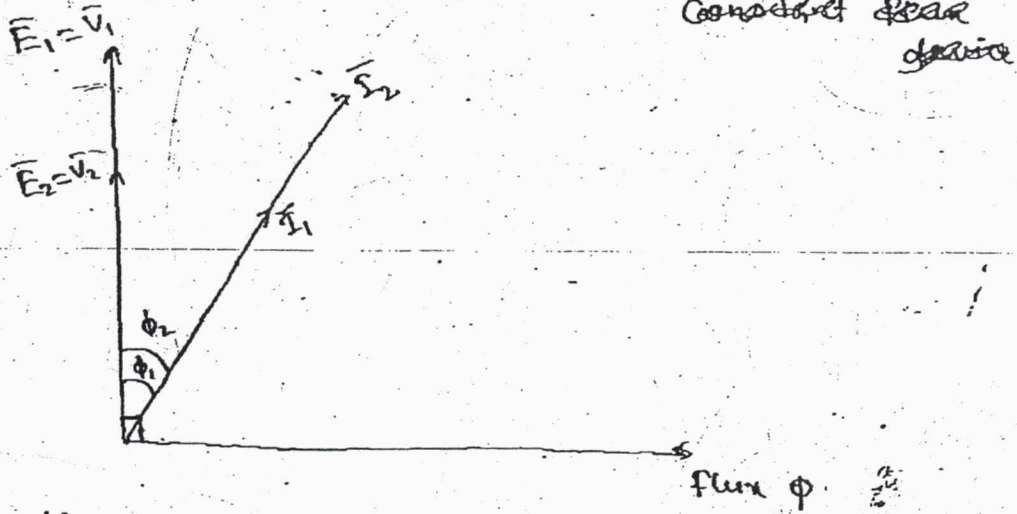
$$\left. \begin{aligned} \Rightarrow \vec{V}_1 \vec{I}_1^* &= \vec{V}_2 \vec{I}_2^* \\ \& \vec{E}_1 \vec{I}_1^* &= \vec{E}_2 \vec{I}_2^* \end{aligned} \right\} \Rightarrow \bar{S}_1 = \bar{S}_2$$




Magnetizing current  $\rightarrow$  2 to 3%.

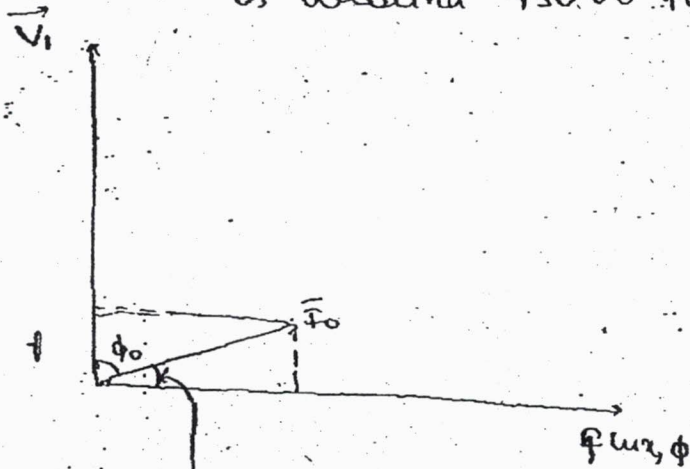
because we do not have any interdigital gap we have a iron core whose permeability is around 150,00 to 20,000.



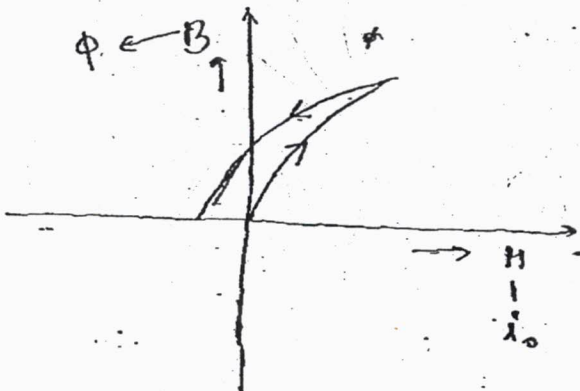
Angle of Hysteretic Advance or Hysteretic lag angle } decided by position of observer



is lead or when observer seen from phi.

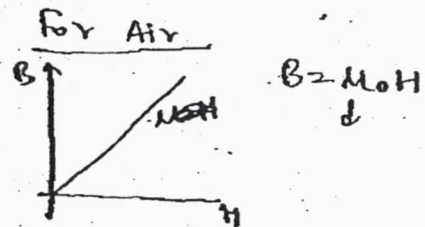



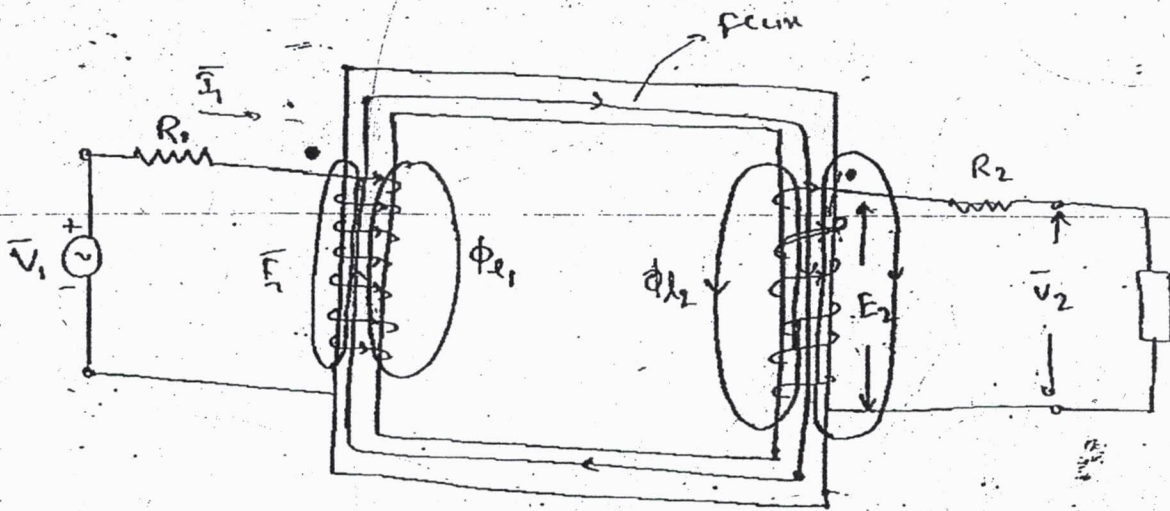


→  $\Phi_{e1}$  is in phase with  $I_1$

$$\therefore B = \mu_0 H$$

↓  
permeability of air

→ Mutual flux is responsible for transfer of power in any electrical machine

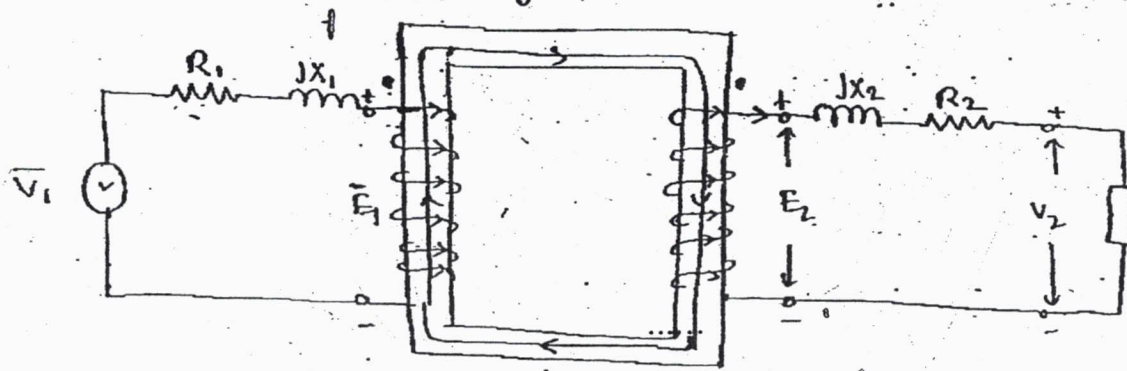→ Leakage flux is only a choke in series which only drops voltage



$$1) \quad \bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + j \bar{I}_2 X_2$$

$$\Rightarrow \bar{E}_2 = \bar{V}_2 + \bar{I}_2 (R_2 + jX_2)$$

$Z_2 = \text{Secondary leakage impedance}$

$$\Rightarrow \bar{E}_2 = \bar{V}_2 + \bar{I}_2 \bar{Z}_2$$

$$2) \quad \bar{E}_1 = a \bar{E}_2$$

3) 
$$\vec{I}_1 = \frac{\vec{I}_2}{a} + \vec{I}_0$$

$$= \vec{I}_2' + \vec{I}_0$$


letero

where  $\vec{I}_0 = \vec{I}_c + \vec{I}_\phi$   
 ↓ phase with  $E_1$       ↓ phase with flux  $\phi$ .

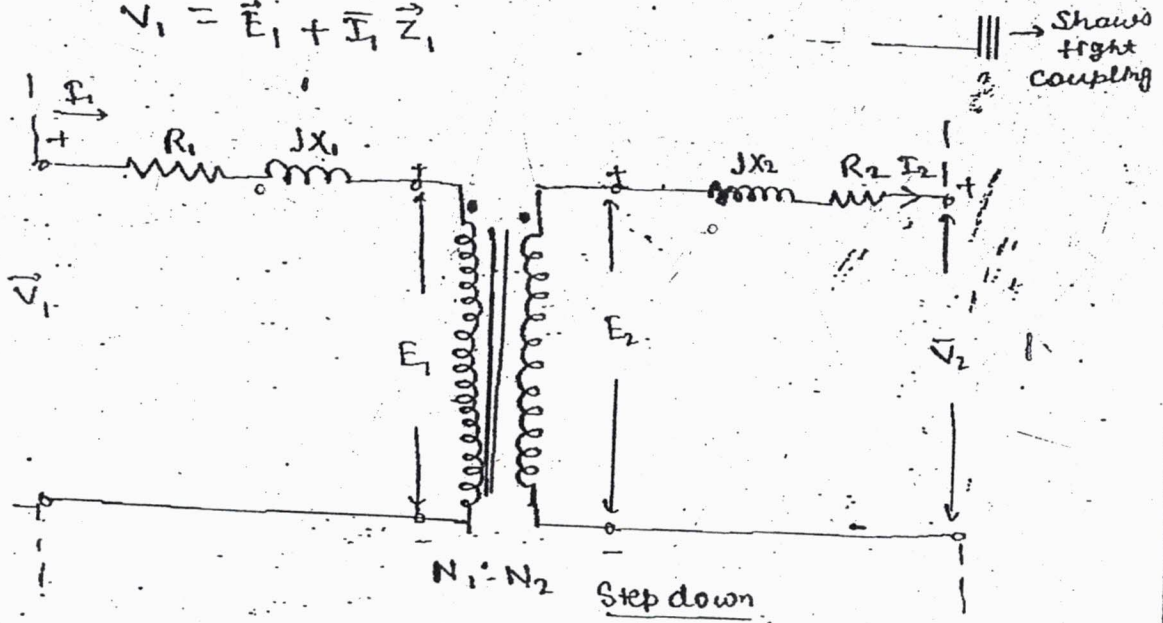
4) 
$$\vec{V}_1 = \vec{E}_1 + \vec{I}_1 R_1 + j \vec{I}_1 X_1$$

$$= \vec{E}_1 + \vec{I}_1 (R_1 + jX_1)$$


$$V_1 = \vec{E}_1 + \vec{I}_1 \vec{Z}_1$$



Lagging PF:

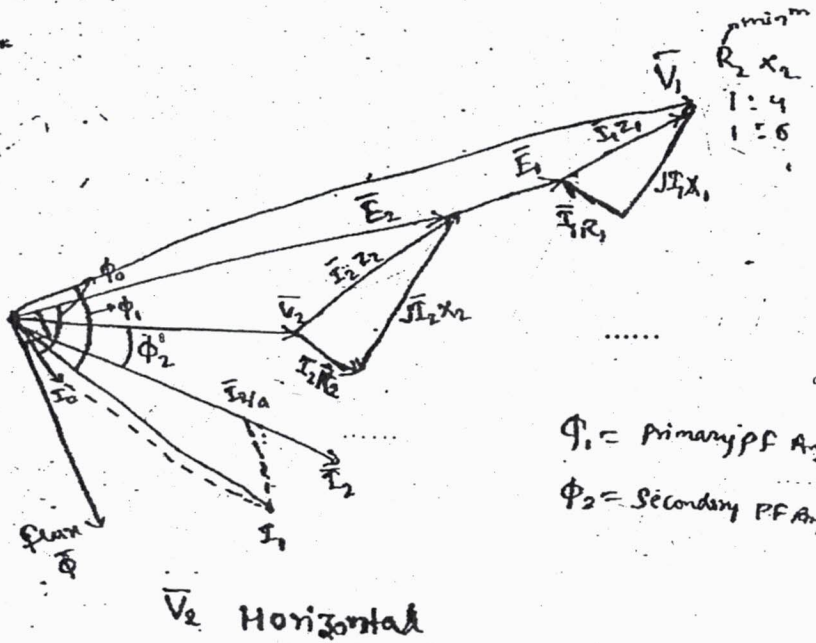


flux horizontal

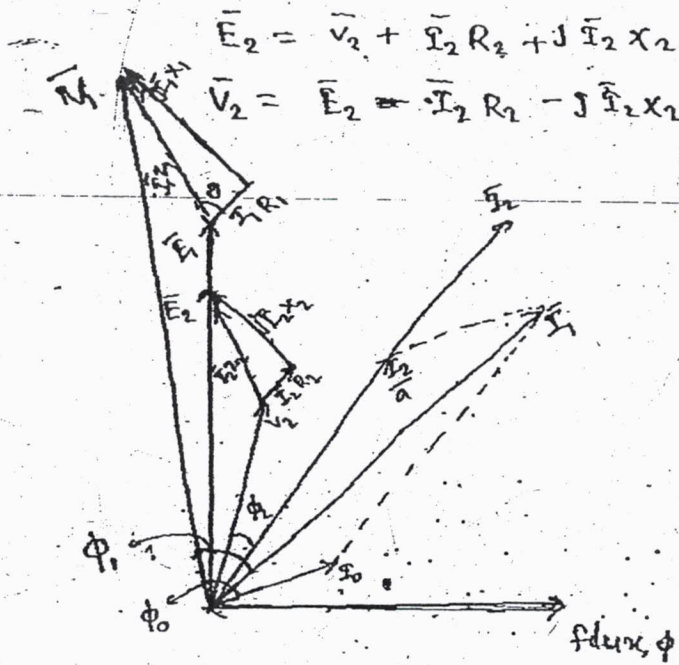

known to unknown

~~secondary voltage~~  
Leading pf

V<sub>2</sub> horizontal

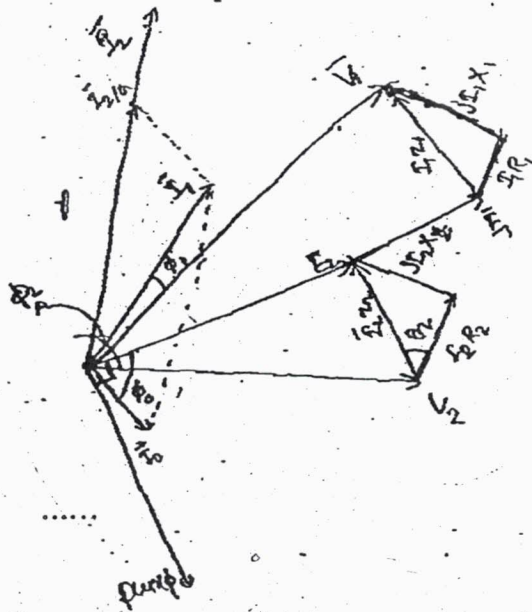

### Equivalent Ckt. of Transformer

\* Representation of any device by standard active, & passive ckt. elements that can be used to analyse and predict the performance of the device is its equivalent ckt.

$$\vec{E}_2 = \vec{V}_2 + \vec{I}_2 R_2 + j \vec{I}_2 X_2$$

Multiplying by  $\frac{N_1}{N_2} = a$

$$\Rightarrow a \vec{E}_2 = a \vec{V}_2 + a \vec{I}_2 R_2 + j a \vec{I}_2 X_2$$

$$\Rightarrow \vec{E}_1 = \vec{E}'_2 = \vec{V}'_2 + \left(\frac{\vec{I}_2}{a}\right) (a^2 R_2) + j \left(\frac{\vec{I}_2}{a}\right) (a^2 X_2)$$


$$= \vec{V}'_2 + \vec{I}'_2 R'_2 + j \vec{I}'_2 X'_2$$

Secondary resistance referred to primary

Secondary leakage reactance referred to primary

$$= \vec{V}'_2 + \vec{I}'_2 (R'_2 + j X'_2)$$
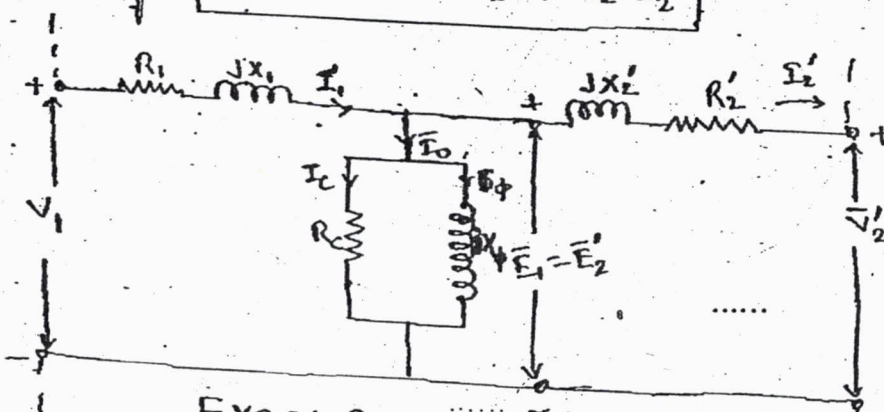
$$\Rightarrow \vec{E}_1 = \vec{E}'_2 = \vec{V}'_2 + \vec{I}'_2 \vec{Z}'_2$$



Because of shape of ckt., it is known as (T-equivalent)

Exact Equivalent Ckt. referred to primary

$R_c$  = core loss equivalent resistance

$X_\phi$  = magnetizing reactance

$X_\phi$  &  $R_c$  is || Element as it


is dependent on applied voltage.

250 kVA, 2500V/250V  
 ↓  
 (delivered o/p power)      o/p terminal voltage  
 ← 1000A      → 1000A

2° referred to 1°  
 $E_1 = a E_2 = E_2'$   
 $I_1' = \frac{I_2}{a}$   
 $R_1' = a^2 R_2$

1° referred to 2°  
 $E_1' = \frac{E_2}{a}$   
 $I_1' = a I_2$   
 $R_1' = R_2/a^2$

2500V / 250V  
 ↓      ↓  
 $aV_2 / V_2$

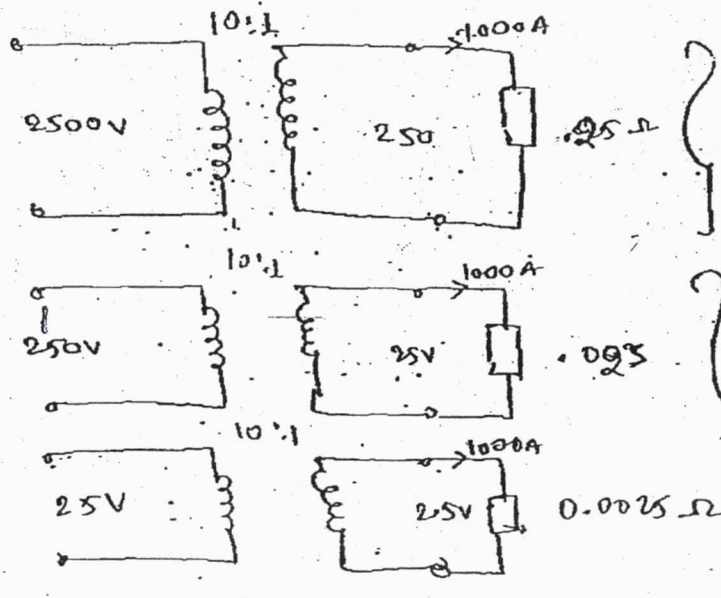

2500  
 10000  
 125

full load  
 full load current but not full load

Full load → Full load current is delivered at rated voltage.



Q. The parameters of equivalent ckt. of 150 kVA, 2400V/240V transformer are.  $R_1 = 0.2 \Omega$   $R_2 = 2 m\Omega$

$X_1 = 0.45 \Omega$   $X_2 = 4.5 m\Omega$

$R_c = 10 k\Omega$   $X_m = 1.55 k\Omega$

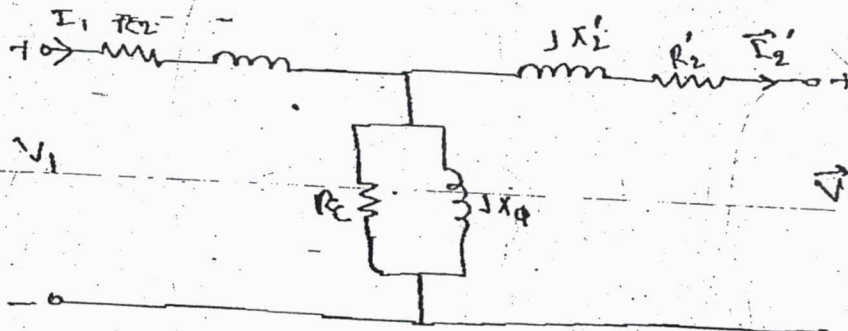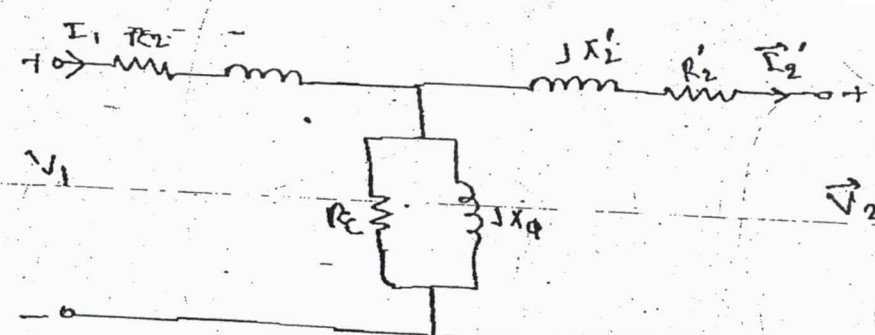Using the ckt. referred to primary, determine primary i/p voltage, i/p current & input pf of x-former operating at rated load with 0.8 lagging pf



Q. 

$$\begin{aligned}\vec{V}_2' &= a V_2 \angle 0^\circ \\ &= 10 \times 240 \angle 0^\circ \\ &= 2400 \angle 0^\circ \text{ Volts.}\end{aligned}$$

$$\begin{aligned}\vec{I}_2 &= \frac{150 \times 10^3}{240} \angle -\cos^{-1}(0.8) \\ &= 625 \angle -36.87^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\therefore \vec{I}_2' &= \frac{\vec{I}_2}{a} = \frac{625}{10} \angle -36.87^\circ \text{ A} \\ &= 62.5 \angle -36.87^\circ\end{aligned}$$

$$\begin{aligned}\vec{Z}_2' &= a^2 \vec{Z}_2 \\ &= (10)^2 [(2 + j4.5) \times 10^{-3}] \\ &= (0.2 + j0.45) \Omega\end{aligned}$$

$$\begin{aligned}\vec{E}_1 &= 2400 \angle 0^\circ + 62.5 \angle -36.87^\circ \times (0.2 + j0.45) \\ &= 2426.92 \angle 0.35^\circ \text{ Volts}\end{aligned}$$


$$\vec{I}_c = \frac{\vec{E}_1}{R_c} = \frac{2426.92 \angle 0.35^\circ}{10 \text{ k}\Omega} = 0.2427 \angle 0.35^\circ \text{ A}$$

$$\vec{I}_\phi = \frac{\vec{E}_1}{jX_\phi} = \frac{2426.92 \angle 0.35^\circ}{1.55 \angle 90^\circ \text{ k}\Omega} = 1.5658 \angle -89.65^\circ$$

$$\begin{aligned}\vec{I}_0 &= \vec{I}_c + \vec{I}_\phi \\ &= 0.2427 \angle 0.35^\circ + 1.5658 \angle -89.65^\circ \\ &= 1.5845 \angle -80.84^\circ\end{aligned}$$

Kingley → Harvard, prof.

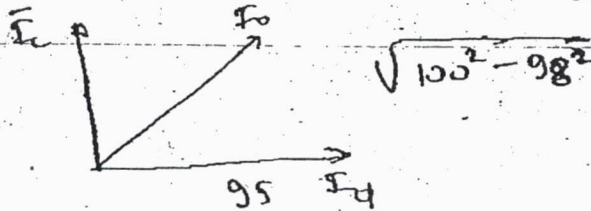$I_Q = 98\%$  of  $I_0$   
 then what is  $I_C = ?$   $I_C = \sqrt{100^2 - 98^2}$   
 $= 15\%$



$$\vec{I}_1 = \vec{I}_2' + \vec{I}_0$$


$$= 63.65 \angle -37.86^\circ \text{ A}$$

$$\vec{V}_1 = \vec{E}_1 + \vec{I}_1 \vec{Z}_1$$

$$= 2426.92 \angle 10.35^\circ + 63.65 \angle -37.86^\circ \times (0.2 + j0.45)$$

$$= 2454.68 \angle +0.69^\circ$$

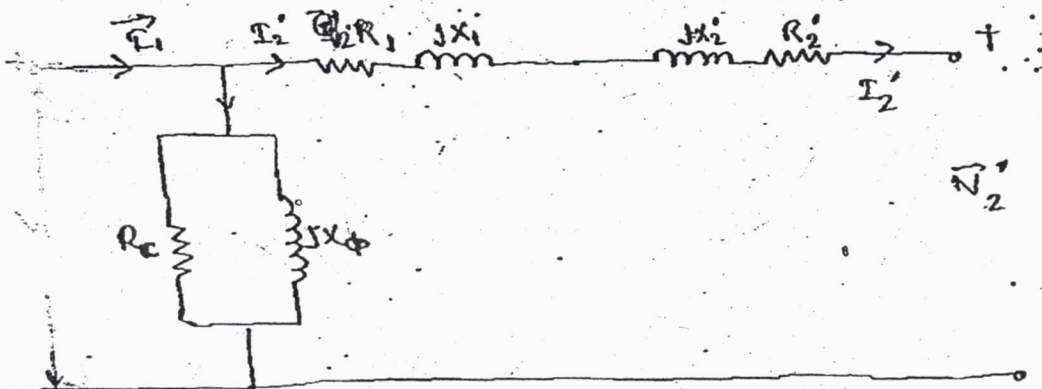
Input PF =  $\cos [0.69^\circ - (-37.86^\circ)]$   
 $= \cos 38.55^\circ \text{ lag.}$   
 $= 0.7821 \text{ lag//}$




(Just like Centimeter ext) - 1st Approx. Ckt. (Due to complexities)

Through magnetic ckt. we can transfer energy very efficient because magnetic flux density is 2500 times more than that of electric field density.

So most of load is magnetic.

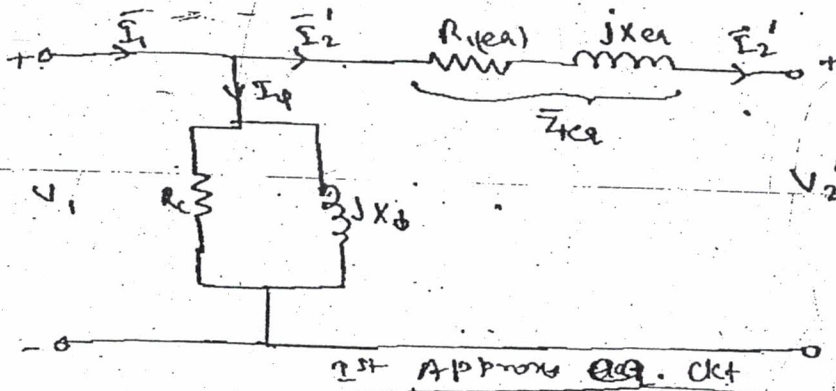
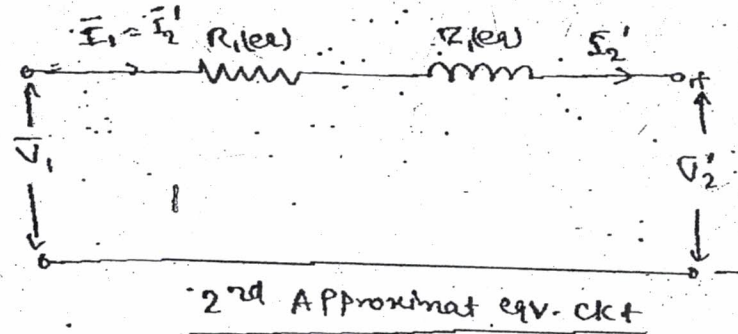
$$\vec{V}_1 = \vec{V}_2' + \vec{I}_2' \vec{Z}_{1eq} = 2453.93 \angle 0.7^\circ \text{ Volt}$$




### # Open ckt. Test or Short ckt. Test
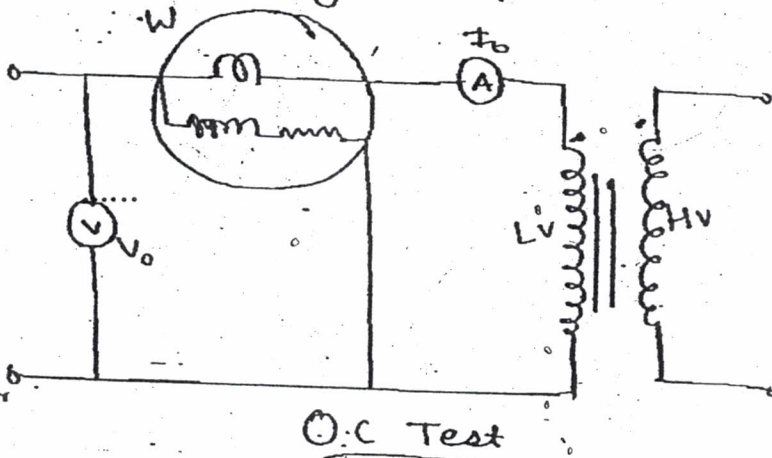
#### Objective of O.C Test

To predict the performance of x-former without actually loading it.

Rated Frequency Adjustable  
Vig AC Supply usually from Auto-transformer




\* O.C Test

\* Open ckt. Test is carried out at rated frequency & rated  $V_{lg}$  to determine the core loss.

\* The core loss is then treated as constant despite minor variation in voltage & frequency during actual operation.

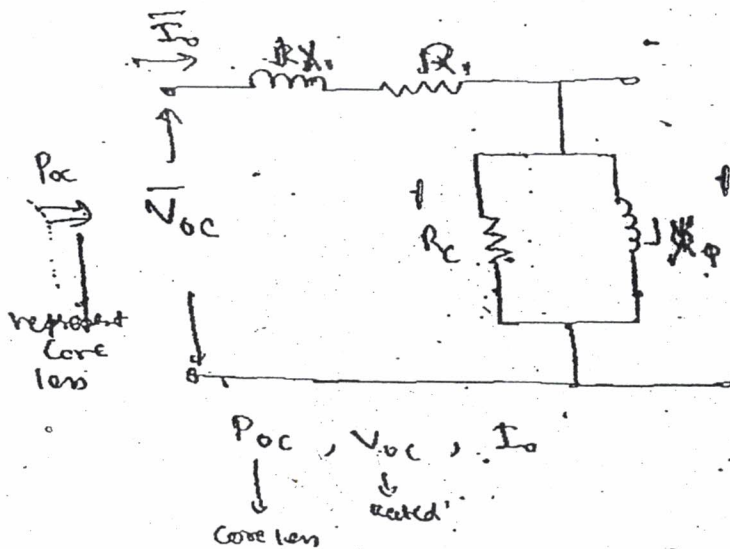\* This test is carried out with instruments placed on the low voltage side and leaving the high  $V_{lg}$  side open ckted. This is because, it is easier to arrange rated voltage at low voltage level rather than at high voltage level. Also it is safer to work on the LV side and the instruments used are of low cost.



$R_1 = 0.5\%$

$X_0 = 5\%$

$I_0^2 R_1$

$= 0.00125\%$

[So we ignore this loss.]

$I_0 = 0.5\% \quad R_1 = 5\%$

$V_{lg \text{ drop}} = I_0 Z_1 = 0.05 \times 0.05 \times 100 = 0.25\% \text{ of } V_{oc}$

(So neglect  $V_{lg}$  drop across  $R_1$ )