

**IES/GATE**

---

**Electrical Engineering**

**VOLUME-VIII**

**Power System-II**



# **Contents**

**Power System-II**

**1-228**




## POWER SYSTEM - 2

BY: BHUPOENDRE SIR
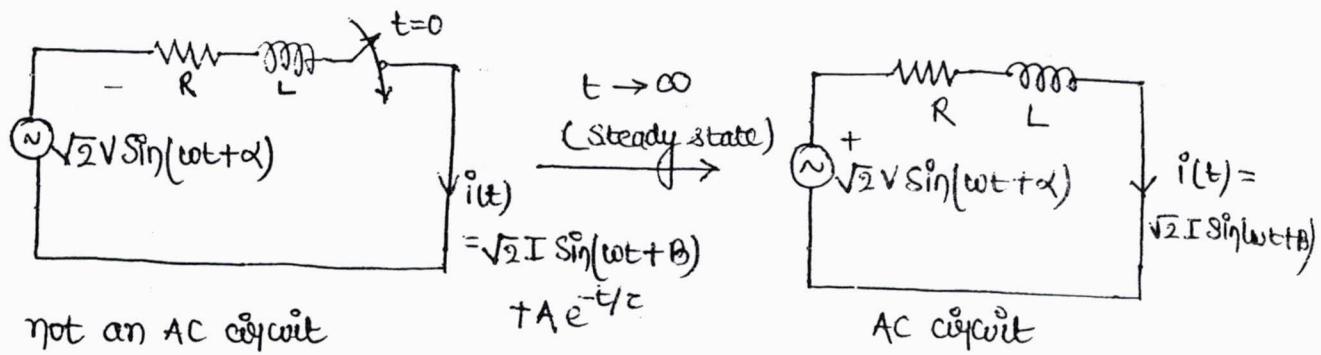
## \* Power analysis of A.C. circuit

A circuit which is in steady state corresponding to a given sinusoidal excitation is called AC circuit.




Responses are non-sinusoidal

Responses are sinusoidal.

→ All the responses of an AC circuit are sinusoids with frequency equal to the source frequency.

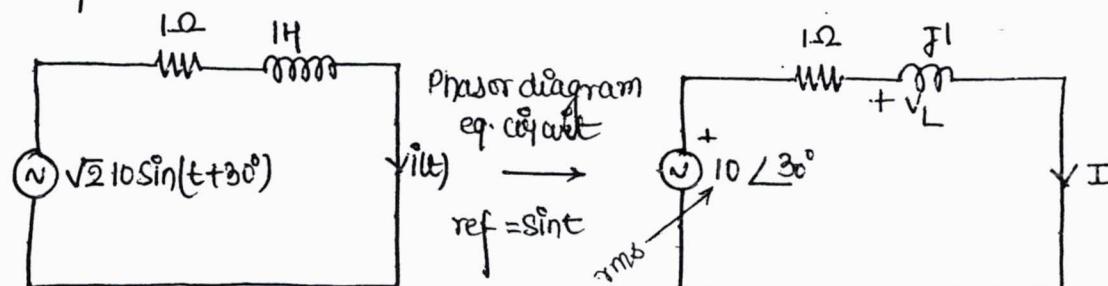→ The magnitude & phase of the response in an AC circuit is determined by phasor technique.




$$i(t) = 10 \sin(t-15^\circ)$$

$$I = \frac{10 \angle 30^\circ}{1+j1} = \frac{10}{\sqrt{2}} \angle -15^\circ$$

$$v_L = \left( \frac{j1}{1+j1} \right) 10 \angle 30^\circ$$
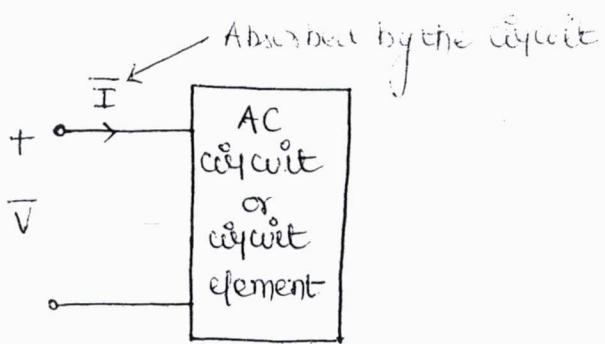
$$= \frac{10}{\sqrt{2}} \angle 75^\circ$$



Complex power absorbed by the circuit or circuit element

$$S = VI^* = P + jQ$$

$P \rightarrow$  Active power / useful power / Avg. power / power absorbed by the ckt or ckt. element (watt)

$Q \rightarrow$  Reactive power / lagging VAR absorbed by the circuit or ckt element (VAR).

$P > 0 \rightarrow$  ckt. absorbs active power

$P < 0 \rightarrow$  ckt. delivers active power


$Q > 0 \rightarrow$  ckt. absorbs reactive power or lagging VAR or lagging current  
or

circuit delivers leading VAR / leading current

$Q < 0 \rightarrow$  circuit delivers reactive power / which is lagging VAR / lagging current  
or

The circuit absorbs leading VAR / leading current

(delivered by the circuit)

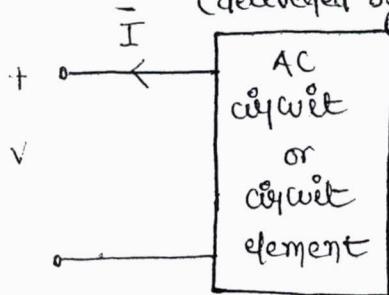

Complex power delivered by the circuit or circuit element -

$$S = VI^* = P + jQ$$

P → Active power delivered by the circuit or circuit element


Q → Reactive power delivered by the circuit or circuit elements

$P > 0 \rightarrow$  circuit delivers active power

$P < 0 \rightarrow$  circuit absorbs active power

$Q > 0 \rightarrow$  circuit delivers reactive power

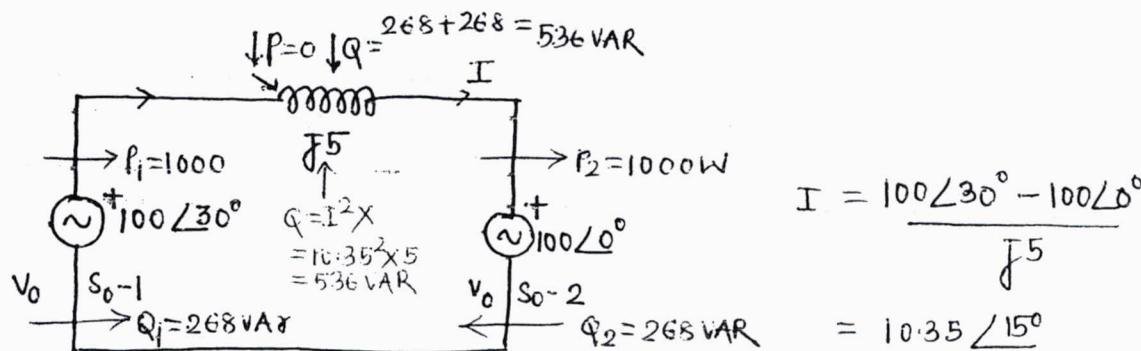$Q < 0 \rightarrow$  circuit absorbs reactive power



Complex power absorbed by V.S.2 -

$$\begin{aligned} S_2 &= (100\angle 0^\circ)(10.35\angle 15^\circ)^* \\ &= 1000 - j268 \end{aligned}$$

V.S.2 →



Absorbs 1000W & delivers 268 VAR

V.S.1 →

Complex power absorbed by V.S.1

$$\begin{aligned} S_1 &= (100\angle 30^\circ)(10.35\angle 15^\circ)^* \\ &= 1000 + j268 \end{aligned}$$

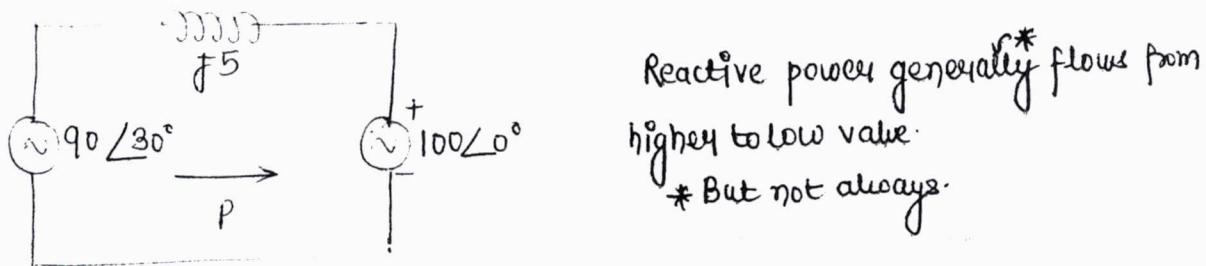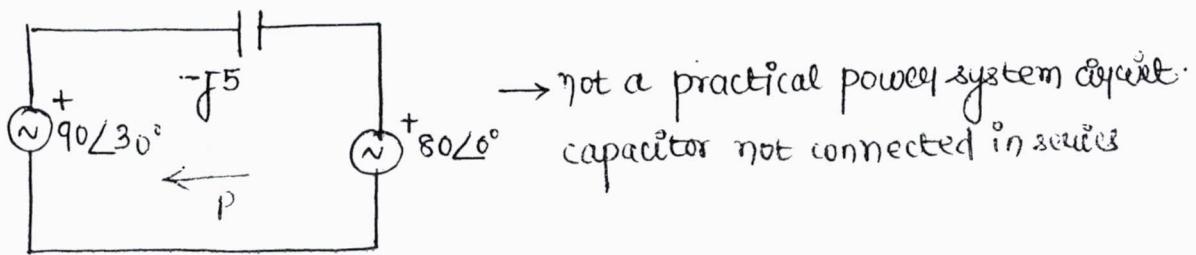Voltage source-1. delivers 1000W & 268 VAR.



In power system (with inductive series branch) active power always flows from leading voltage source towards lagging voltage source.

$$\bar{V} = V \angle 0$$

$$Z = R + jX$$

$$\Theta = |Z| \angle \theta$$

$$|Z| = \sqrt{R^2 + X^2}$$


$$\Theta = \tan^{-1} \frac{X}{R}$$

Complex power absorbed by  $Z = R + jX$

$$S = \bar{V} \bar{I}^* = V I \angle \theta = P + jQ$$

$$P = V I \cos \theta = V I \frac{R}{|Z|} = I^2 R$$

$$Q = V I \sin \theta = V I \frac{X}{|Z|} = I^2 X$$

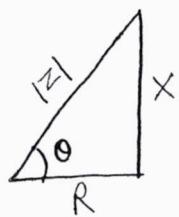

$$\cos \theta = \frac{R}{|Z|}$$

$$\sin \theta = \frac{X}{|Z|}$$

Impedance Triangle

$$\begin{array}{l}
 S = I^2 |Z| \\
 = VI \\
 P = I^2 R \\
 Q = I^2 X
 \end{array}$$




$$P.f. = \cos \theta = \frac{P}{S}$$

$R > 0 \Rightarrow P > 0$  ( $Z = R + jX$  can't deliver active power)

$X > 0$  (Inductive)  $= Q > 0$  Inductive circuit absorbs reactive power

$X = 0$  (Resistive)  $= Q = 0$

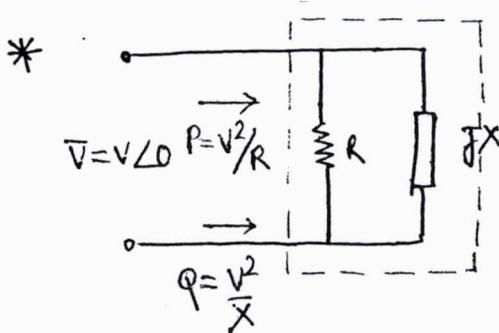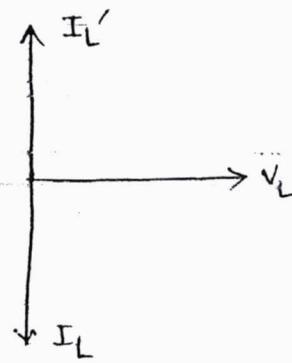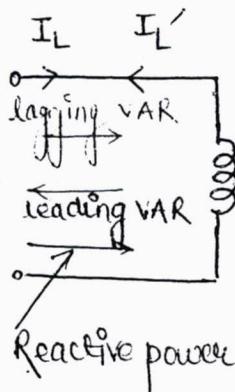$X < 0$  (Capacitive)  $\Rightarrow Q < 0$  Capacitive circuit delivers reactive power




### Balance 3-φ circuit / concept of phase sequence

A polyphase system is said to be balance if -

- › The magnitude of corresponding quantities are equal in each phase.
- › The phase difference between corresponding quantities is given by  $\frac{360^\circ}{n}$ .

$$\frac{360^\circ}{n} \rightarrow n=2$$


$$90^\circ \rightarrow n=2$$

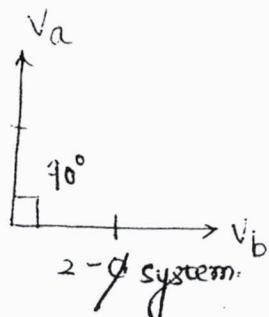



The currents in two phases of a 2-φ system is given below. Find the relation between  $\phi_1$  &  $\phi_2$  so that these current represents a balance 2-φ system.

$$i_a = \sqrt{2} I \sin(\omega t - \phi_1)$$
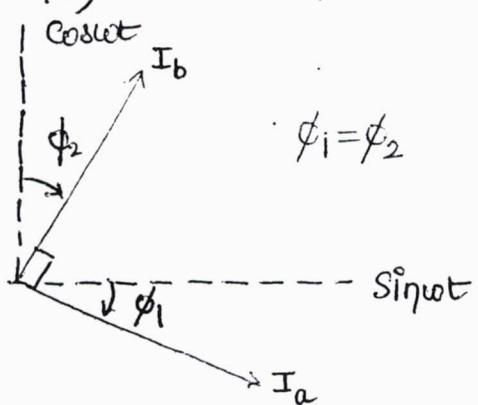
$$i_b = \sqrt{2} I \cos(\omega t - \phi_2)$$





\*

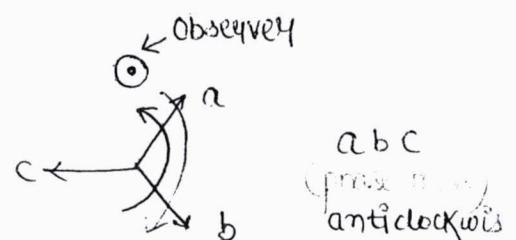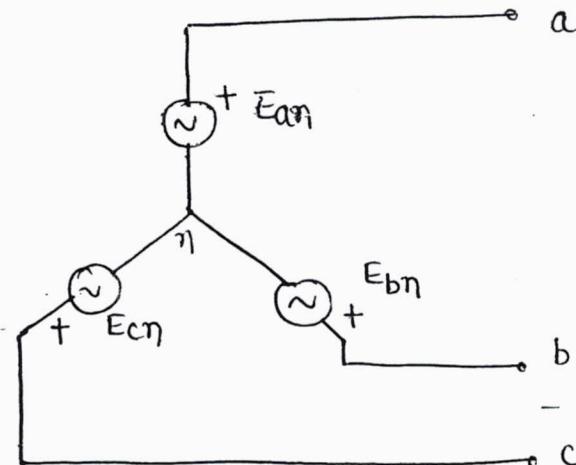


→ observer moves clockwise to detect phase sequence.

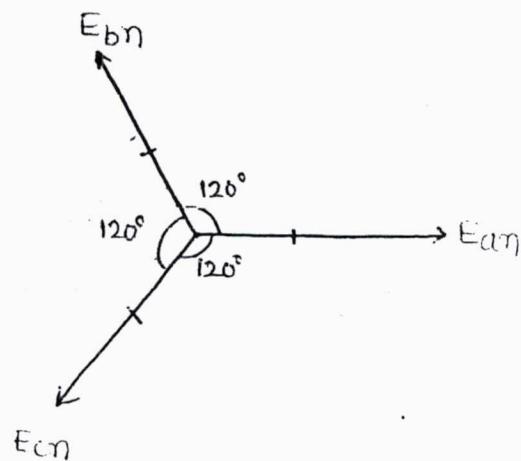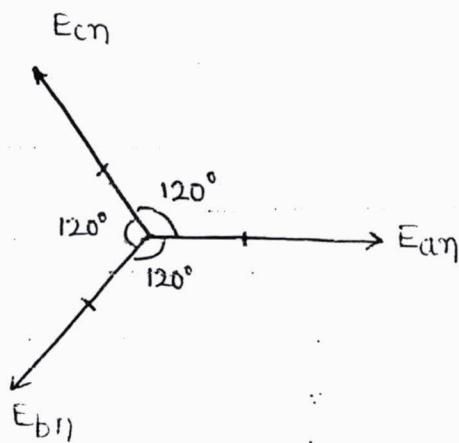
→ The 3-φ voltage source represents a synchronous machine.



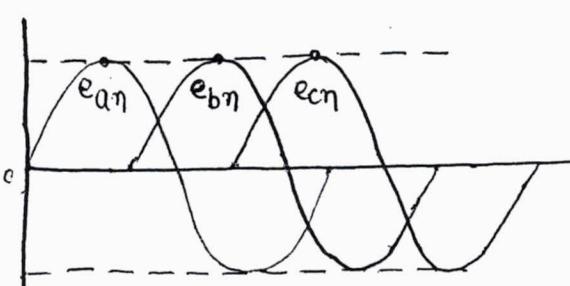
→ Both phasor diagram represents balance condition but they do differ in phase sequence.



PS  $\Rightarrow$  abc

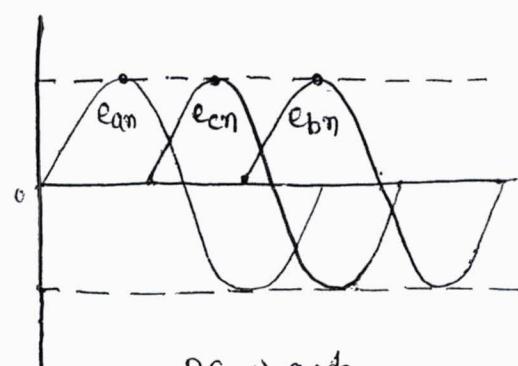


PS  $\Rightarrow$  acb

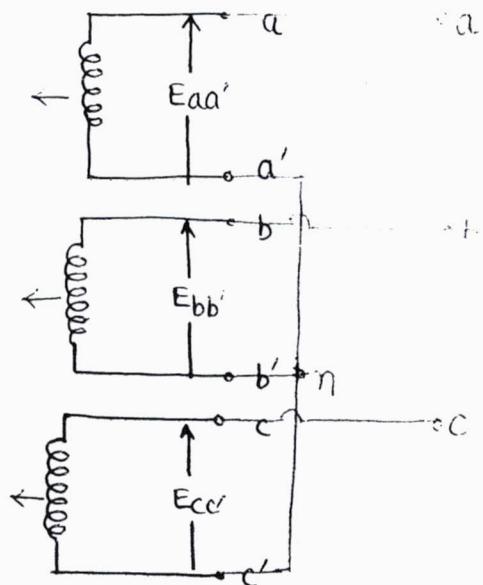

Identical winding for all three phases to produce equal magnitude of voltage in all three phases.

Phase sequence  
= acb

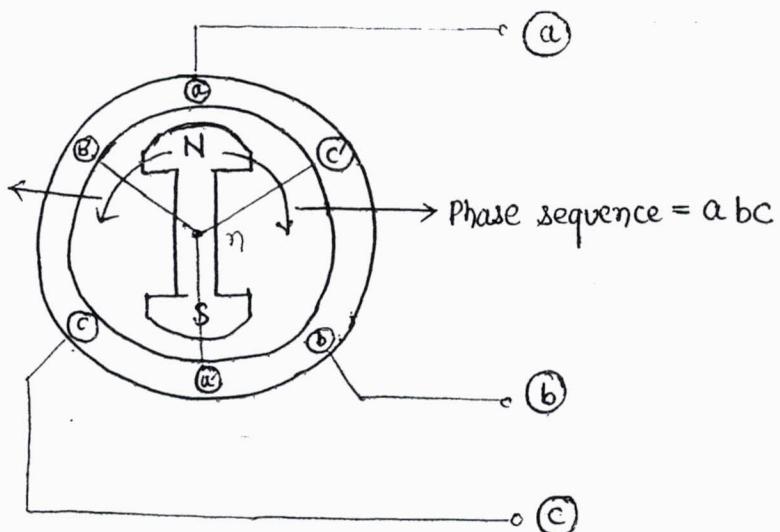


$$\theta_e = \frac{P}{2} \theta_M$$

Only two type of phase sequence (abc & acb) is possible in 3-ph system.

Theoretically phase sequence can be reversed by reversing the direction of rotation of the rotor but practically this is not feasible.

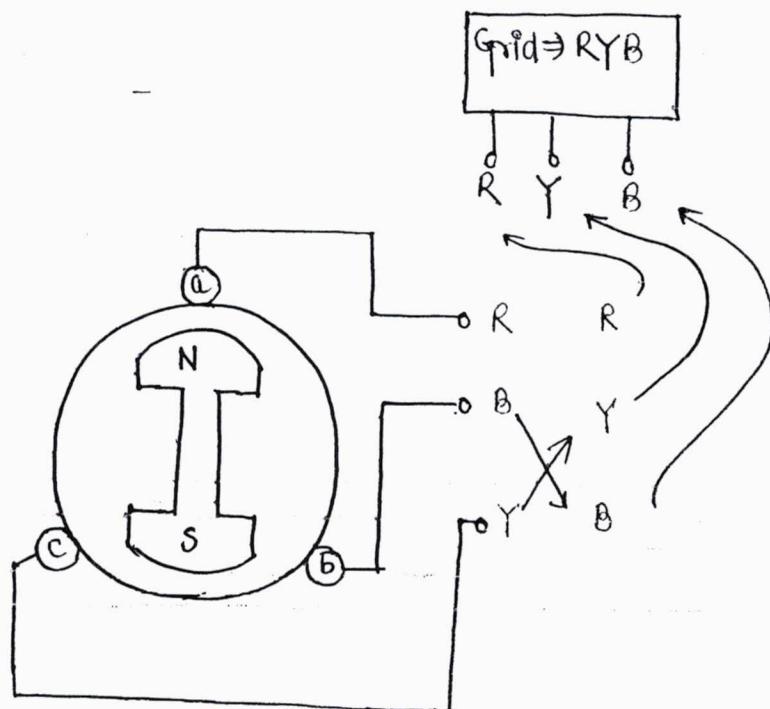
- If field winding excitation is reversed phase sequence will not be reversed.
- \* Phase sequence of the machine is practically reversed by interchanging any two terminals of a machine.



Otherwise heavy circulating current will happen

In a particular power system all the machines operate at same phase sequence & it is the sequence of whole system.

\* Analysis of Balance 3-φ circuit

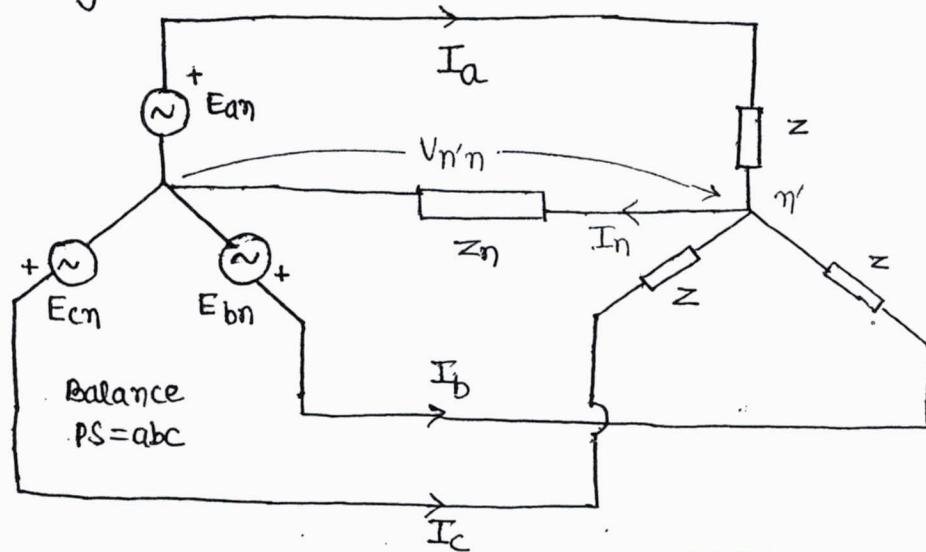

$$\rightarrow I_a + I_b + I_c - I_\eta = 0$$

$$\rightarrow \frac{E_{an} - V_{n'n}}{Z} + \frac{E_{bn} - V_{n'n}}{Z} + \frac{E_{cn} - V_{n'n}}{Z} - \frac{V_{n'n}}{Z_\eta} = 0$$

$$\frac{1}{Z} (E_{an} + E_{bn} + E_{cn}) - \left( \frac{3}{Z} + \frac{1}{Z_\eta} \right) V_{n'n} = 0$$

Since, the source is balanced

$$E_{an} + E_{bn} + E_{cn} = 0 \Rightarrow V_{n'n} = 0$$

$$I_\eta = 0$$

$$I_a = \frac{E_{an}}{Z}$$

$$I_b = \frac{E_{bn}}{Z}$$

$$I_c = \frac{E_{cn}}{Z}$$

$$E_{an} = 100 \angle 0^\circ$$

$$P.S. = abc$$

$$E_{bn} = 100 \angle -120^\circ$$

$$Z = 10 \angle 30^\circ$$

$$E_{cn} = 100 \angle +120^\circ$$

$$I_a = \frac{E_{an}}{Z} = \frac{100 \angle 0^\circ}{10 \angle 30^\circ} = 10 \angle -30^\circ$$

$$I_b = \frac{E_{bn}}{Z} = \frac{100 \angle -120^\circ}{10 \angle 30^\circ} = 10 \angle -150^\circ$$

$$I_c = \frac{E_{cn}}{Z} = \frac{100 \angle +120^\circ}{10 \angle 30^\circ} = 10 \angle +90^\circ$$


$$PS = abc$$

} .

\* In a balance 3-φ circuit

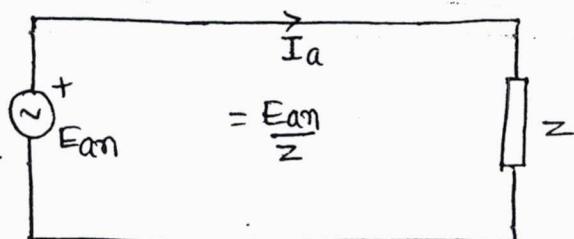- i) All the responses are balance & they have phase sequence as of the sources in the circuit.
- ii) All the neutrals are at same potential & hence there will be no current in the neutral connection irrespective of the value of  $Z_n$ . Hence the neutral connection can be replaced by O.C. or S.C. but we prefer S.C. to show the fact that neutrals are at same potential.
- iii) All the three phases are decoupled i.e. independent of each other hence the analysis can be done on individual phase basis.



→ For the analysis of phase 'a' of the balance circuit phase A equivalent circuit drawn as follows:-



Phase-a equivalent circuit / per phase eq circuit

If phase-a quantity is computed from phase-a equivalent circuit Phase-B & phase-C quantities can be determined directly with the help of phase sequence of the source.

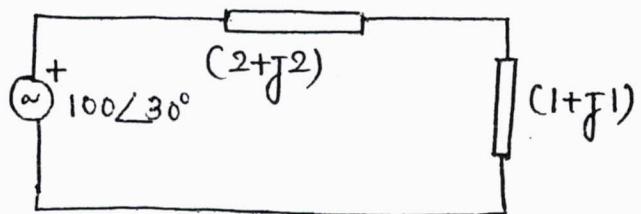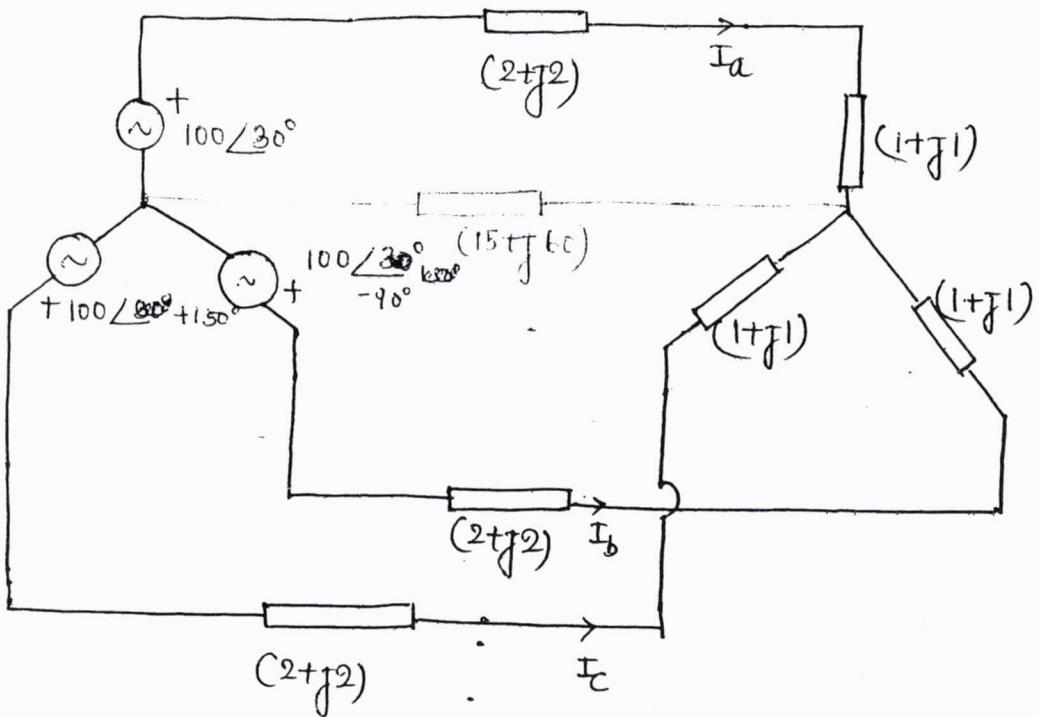"The analysis of a balance 3-φ circuit is always done on per phase basis".





per phase equivalent circuit

$$I_a = \frac{100\angle 30^\circ}{(3+j3)} = 23.5\angle -15^\circ$$

$$I_b = 23.5\angle -135^\circ$$

$$I_c = 23.5\angle 105^\circ$$

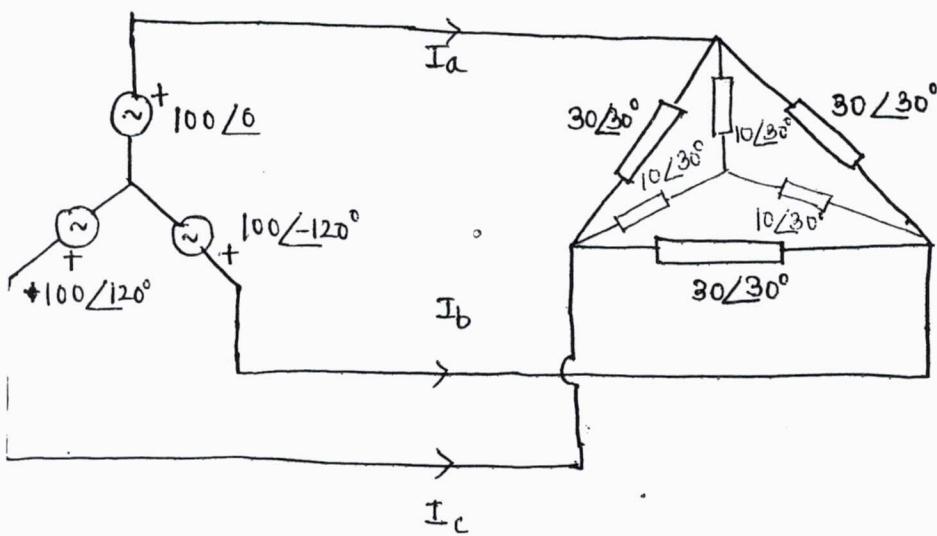

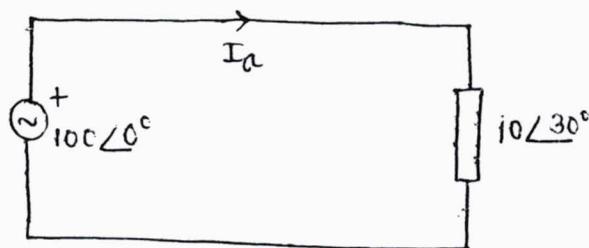

per phase equivalent circuit

$$I_a = \frac{100\angle 0^\circ}{10\angle 30^\circ} = 10\angle -30^\circ$$


$$I_b = 10\angle -150^\circ$$

$$I_c = 10\angle 90^\circ$$




Note:

For the analysis of the balanced 3-Ø circuit on per phase basis all the sources & loads of the circuits must be either stay connected or converted into equivalent star.

### \* Δ to Y source transformation

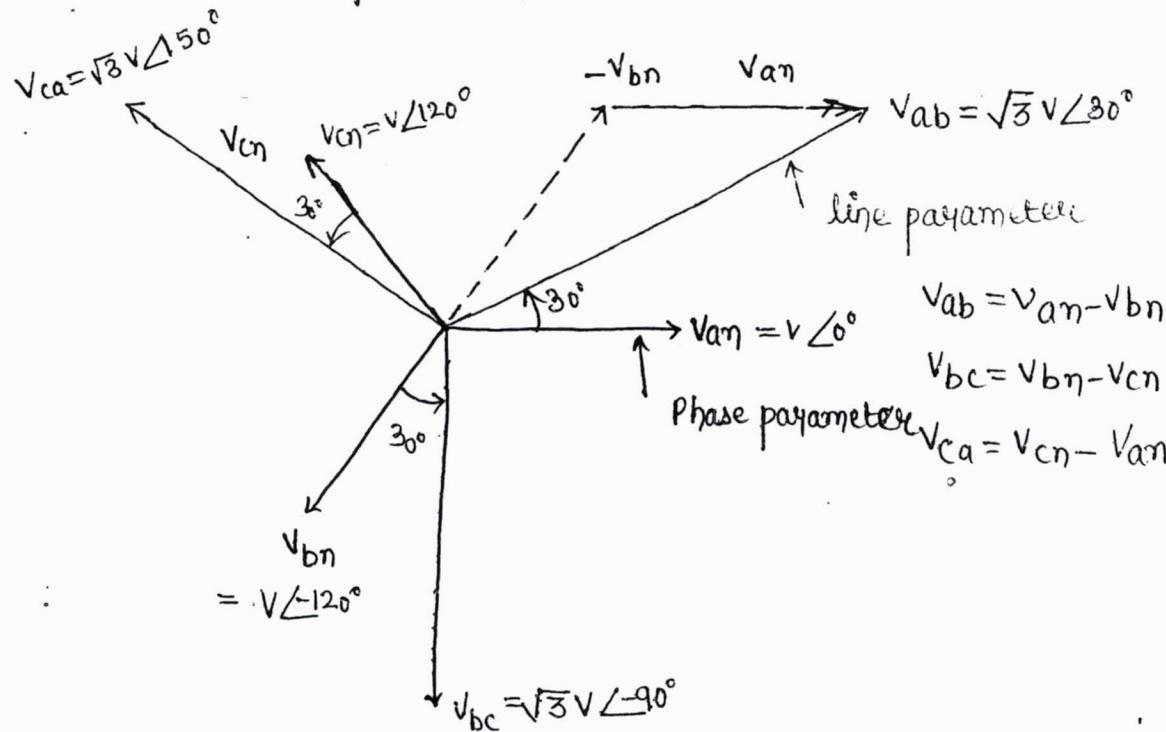

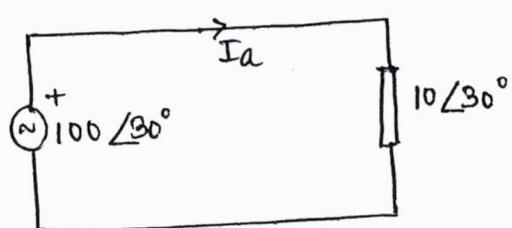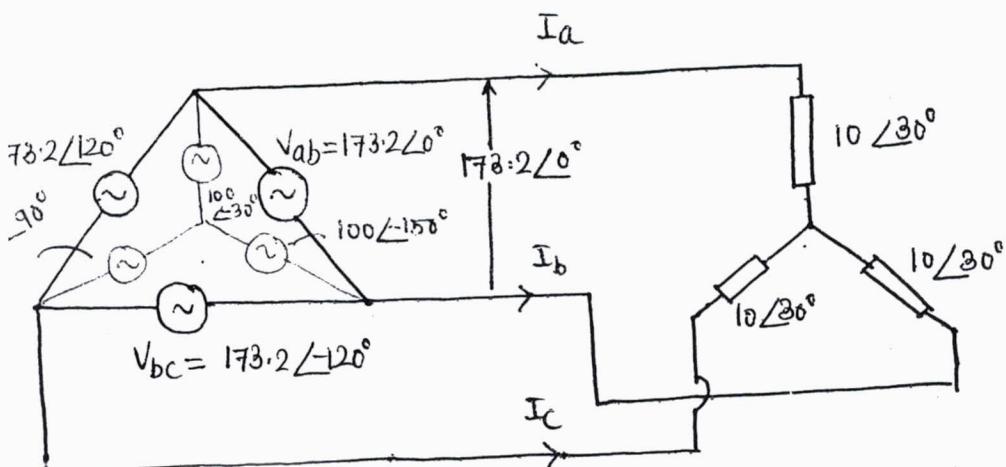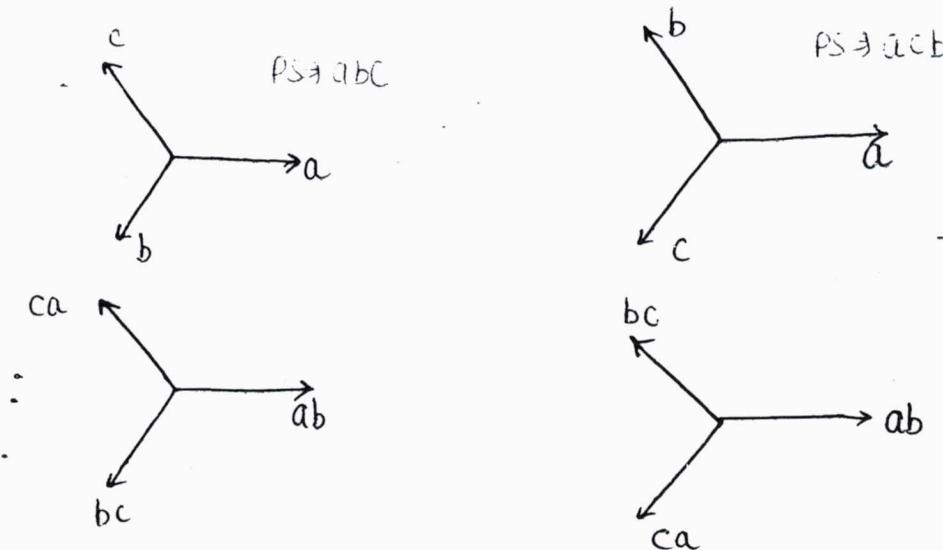
1) In a balanced 3-phase system line voltage is  $\sqrt{3}$  times of phase voltage & lags the phase voltage by  $30^\circ$ .




$$I_a = \frac{100 \angle -30^\circ}{10 \angle 30^\circ} = 10 \angle -60^\circ$$

$$I_b = 10 \angle -180^\circ$$

$$I_c = 10 \angle 60^\circ$$

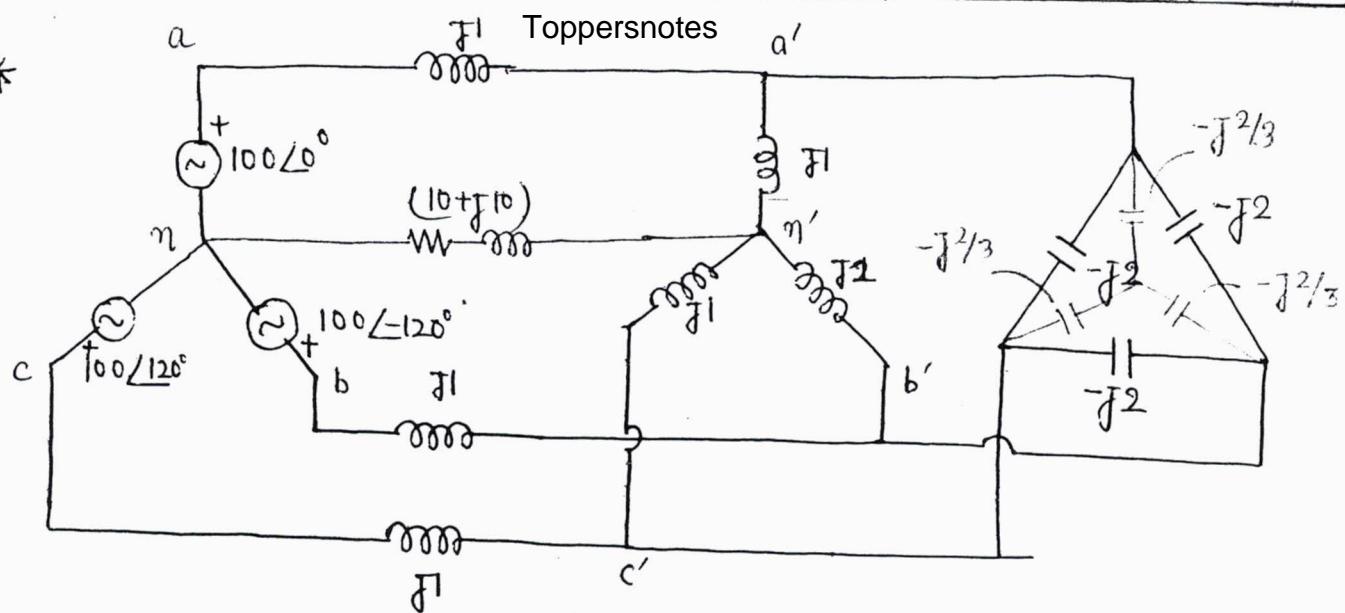

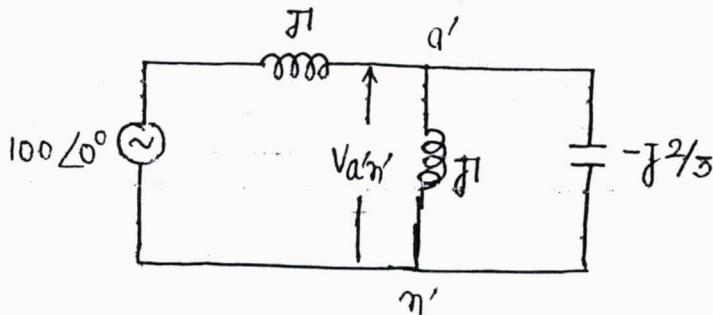Determine phase voltage for the star connected load & phase current for the Δ-connected load.



$$V_{a'\eta'} = \left( \frac{J1 || -J2/3}{J1 + J1 || -J2/3} \right) 100\angle 0^\circ = 200\angle 0^\circ$$

$$V_{b'\eta'} = 200\angle -120^\circ$$

$$V_{c'\eta'} = 200\angle +120^\circ$$

Method 1

$$V_{a'b'} = 200\sqrt{3}\angle 30^\circ$$

$$\text{P. } I_{a'b'} = \frac{V_{a'b'}}{-J2} = 173.2\angle 120^\circ$$

$$I_{b'c'} = 173.2\angle 0^\circ$$



$$I_{c'a'} = 173.2\angle 4240^\circ$$

method 2

$$I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

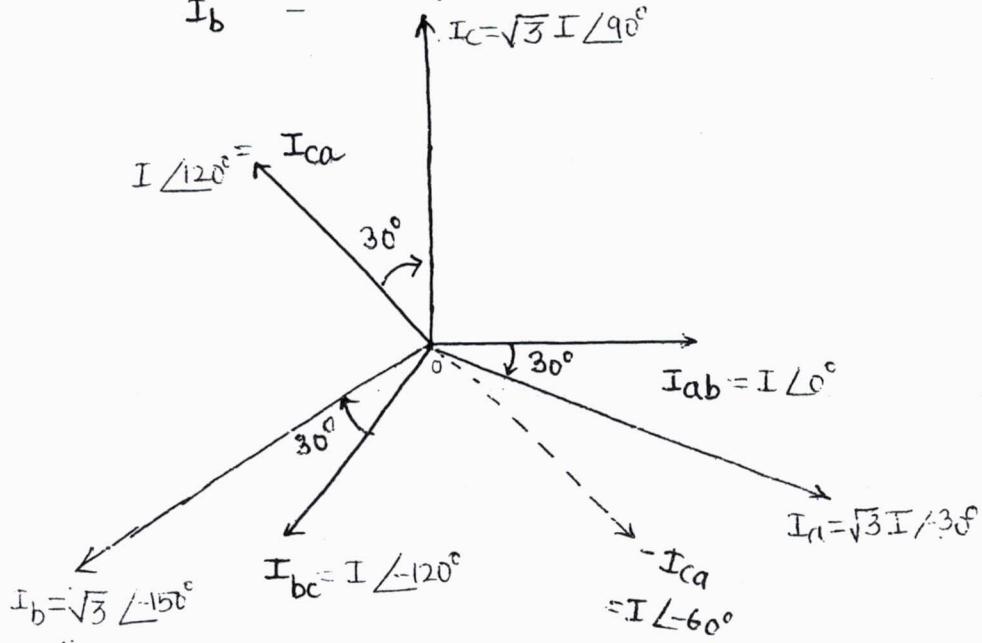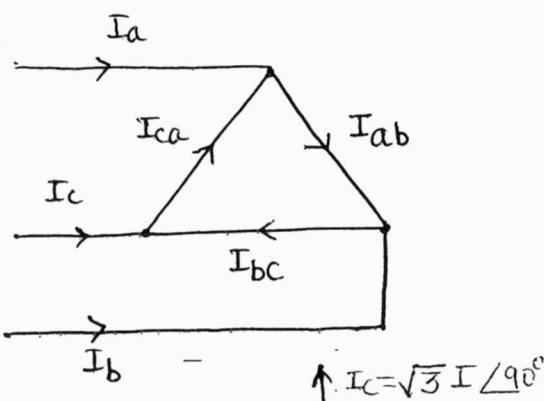

ote

In a balanced  $\Delta$  connected system line current is  $\sqrt{3}$  times of phase current & lags the phase current by  $30^\circ$ .

line current for the  $\Delta$  load —

$$I_a' = \frac{V_a'n'}{-\sqrt{2}/3} = \frac{200 \angle 0^\circ}{-\sqrt{2}/3} = 300 \angle 90^\circ$$

phase current by for  $\Delta$ -load —

$$I_{a'b'} = 173.2 \angle 120^\circ$$

$$I_{b'c'} = 173.2 \angle 0^\circ$$

$$I_{c'a'} = 173.2 \angle 240^\circ$$