

IES / GATE

**Electronics &
Telecommunication
Engineering**

VOLUME-III

Network Theory

Contents

Network Theory

1-283

NETWORK THEORY

1. Basics
2. Steady state A.C. Circuits [Resonance]
3. Theorems
4. Transients
5. Two-port
6. Graph Theory
7. Magnetic Coupled Circuits (*Not in Syll*)
8. Filters (*Not in Syll*)

} frequently asked
-

• Fundamentals of Electric Circuits :-

by Alexander & Sadiku | *only exercises!

- Engg Circuit Analysis :- Hayt & Kemmerly
- Network Analysis [Transients and two port \Rightarrow conventional] :- Van Valkenberg.

1] Gate - EC (

Problems

3] Workbook

2] IAS

2] IES < Memory (40% repeated) Problems

4] Home work

6] Text - series $\left\{ \begin{array}{l} \rightarrow \text{old} \\ \rightarrow \text{new} \end{array} \right.$


* goo.gl/2XnUx3 \rightarrow sadiku $\left\{ \begin{array}{l} \rightarrow \text{Textbook} \\ \rightarrow \text{soln} \end{array} \right.$

* goo.gl/HWKRZ3 \rightarrow Home work (Nodal & Mesh analysis)


* goo.gl/6Fa34E \rightarrow steady state + Theorems

* goo.gl/dTnhu8 \rightarrow RL, RC, RLC \rightarrow conv.

• Network vs Circuit :->

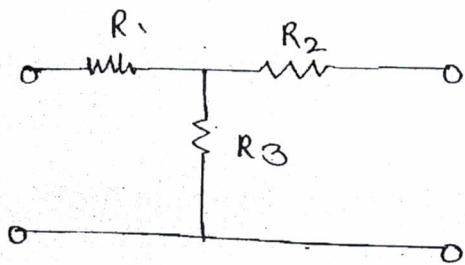

T-Network

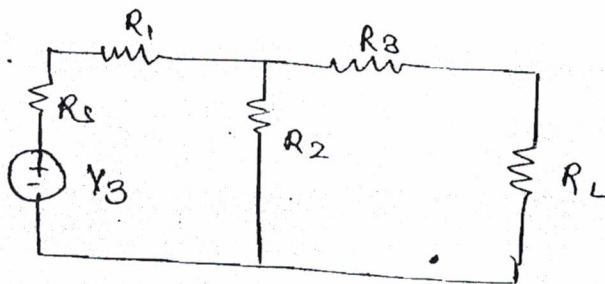

Network or circuit


- Network is a combination of elements, it may or may not consist of closed path.
- Circuit is a combination of elements and it should consist of closed path.
- All circuits are Network, but all Networks are not circuits.

• $q = -1.602 \times 10^{-19} \text{ C}$

$I = \frac{dQ}{dt} \frac{\text{C}}{\text{s}} \text{ or } \text{A}$

rate of flow of charge with time

← I conventional current (assumed dir)

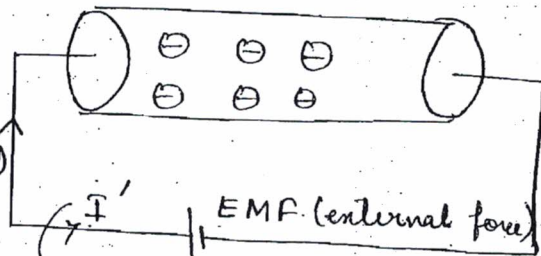

EMF (external force)
natural current (\$e^-\$ flow dir)

[higher pot → lower pot]

$Q = \int I \cdot dt$

In KCL, KVL we always use conventional direction

$|I| = I'$ but opposite in direction.

$Q = \int_{-\infty}^t I \cdot dt = \int_{-\infty}^0 I \cdot dt + \int_0^t I \cdot dt \text{ or } Q = Q_0 + \int I \cdot dt$

$V = \frac{dW}{dQ} = \frac{J}{C} \text{ or Volt}$


$P = \frac{dW}{dt} \frac{J}{s} \text{ or Watt}$

initial charge
→ time rate of energy.

$= \frac{dW}{dQ} \times \frac{dQ}{dt}$

$P = VI = I^2 R = \frac{V^2}{R} = \frac{6V^2}{R} = I^2/6$

$\left[\frac{1}{R} = 6 \right]$

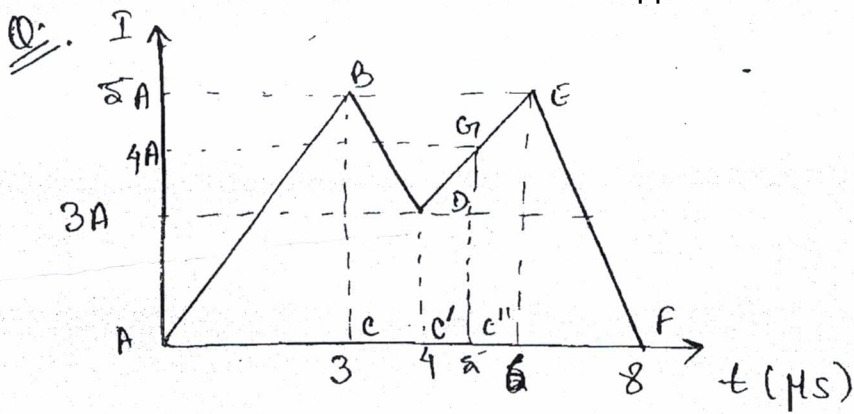

Find charge acquired by cap in $5 \mu\text{sec}$

$\Rightarrow Q = \int I dt$

- 2 methods: ① Developing mathematical eqⁿ
 ② Finding area under curve.

2. $Q = \int I dt$


$= \Delta ABC + \square BDC'C + \Delta C'DGC''$

$= \frac{1}{2} (3 \times 5) + \frac{1}{2} \times (3+5) \times 1 + \frac{1}{2} \times (3+4) \times 1$

* Area of Trapezoid = $\frac{1}{2} \times (\text{sum of ht of 2 sides}) \times \text{dist b/w sides}$

* DE - linear, slope constant $m=1 \therefore$ at $5 \mu\text{s}$; $I = 4 \text{ A}$

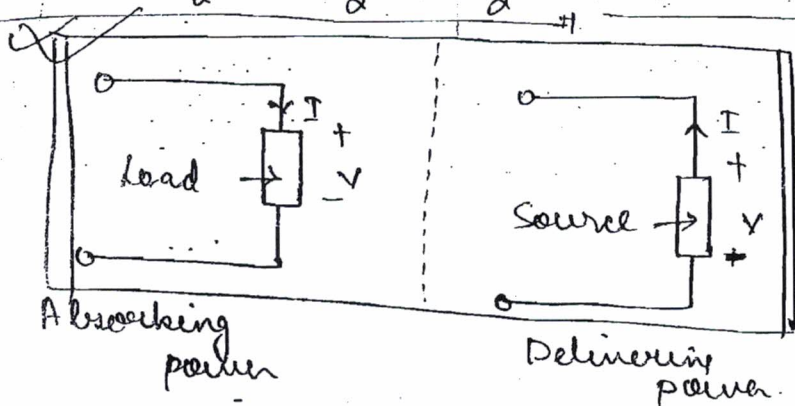
$= \frac{1}{2} \times 15 + \frac{1}{2} \times 8 + \frac{1}{2} \times 7 = 7.5 + 4 + 3.5 = 15 \mu\text{C}$



\Rightarrow Absorbing + Delivering
Source / load (element)

* When the current is entering at the terminal element is absorbing power.

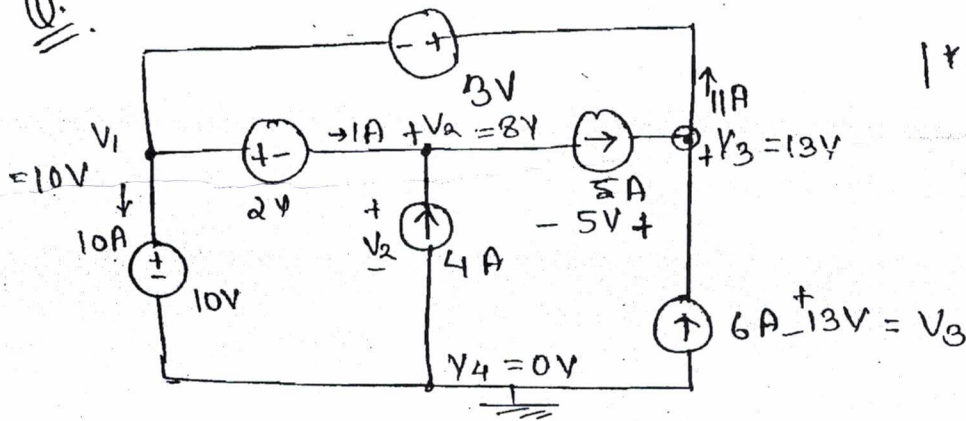* When the current is leaving from the terminal element is delivering power



! To find power, find voltage & current of each element *

Find power of each element of the circuit shown.

\Rightarrow potential between V_1 & $gnd = 10V \therefore V_1 = 10V$

at node V_1 & V_2 : $V_1 - V_2 = 2V \therefore V_2 = 8V$

at node V_1 & V_3 : $V_3 - V_1 = 3V \therefore V_3 = 13V$

In 4A: $P = 4 \times 8 = 32W$ (Delivering)

In 6A: $P = 6 \times 13 = 78W$ (Delivering)

In 5A: $P = 5 \times 5 = 25W$ (Delivering)

current leaving
+ve terminal

In 3V: $P = 11 \times 3 = 33W$ (Absorbing)

In 2V: $P = 1 \times 2 = 2W$ (Absorbing)

In 10V: $P = 10 \times 10 = 100W$ (Absorbing)


if entering +ve
terminal or going
from lower to higher
pot.

$$(P_T)_{\text{Absorbing}} = (P_T)_{\text{Delivering}}$$

$$P_{T \text{ del}} = 32 + 78 + 25 = 135W$$

$$P_{T \text{ abs}} = 33 + 2 + 100 = 135W$$

verified.

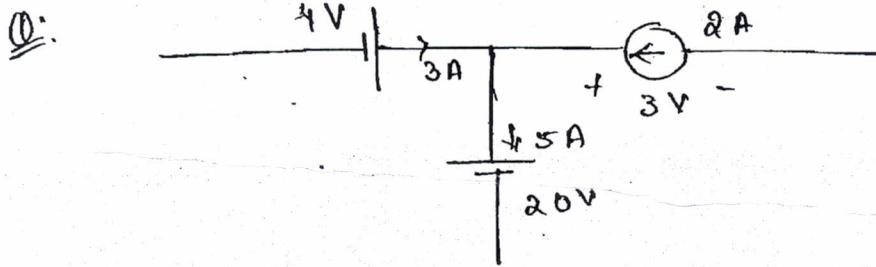

Find total power absorbed in the figure shown.

In 4V:- $P = 4 \times 3 = 12W$ (Del) = $-12W$ (Abs)

In 2A:- $P = 2 \times 3 = 6W$ (Del) = $-6W$ (Abs)

In 20V:- $P = 20 \times 5 = 100W$ (Absorbing)

$$* P_T = 82W \text{ (Absorbing)} *$$

• The capacity to do work is called energy.

$$W = \int_0^t P dt \quad \text{watt-sec or Joule}$$


Q. A fully charged mb. phone is good for 10min talktime. During talktime battery delivers a constant current of 2A. Find energy on the battery during talktime.

$$\begin{aligned} \Rightarrow W &= \int_0^t P dt = \int_0^t VI dt \\ &= I \int_0^t V \cdot dt \quad I = 2A \text{ (constant)} \end{aligned}$$

$$= 2 \times \frac{1}{2} \times (12 + 10) \times 600$$


$$= 22 \times 600$$

$$= 13200 = 13.2 \text{ KJ}$$

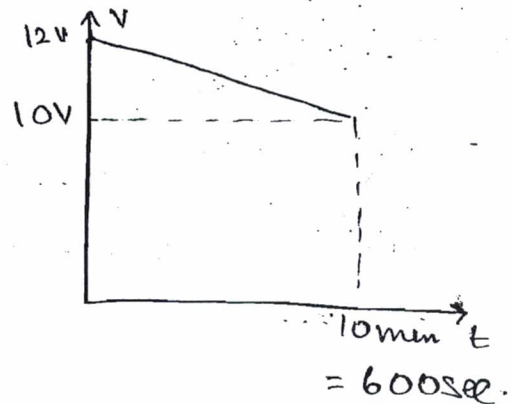

Classification of Elements :-

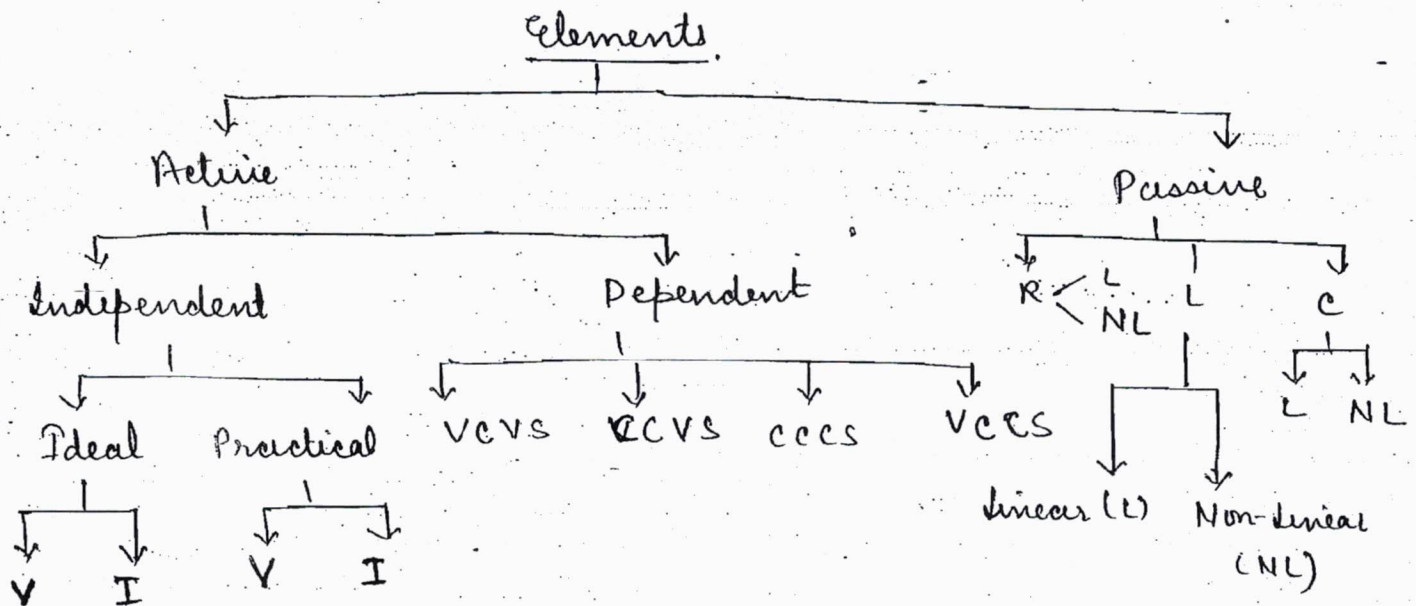1. Active & Passive Elements:-
2. Linear and Non linear Elements
3. Unidirectional and bi-directional elements
4. Time Variant and Invariant
5. Lumped & Distributed



• **ACTIVE ELEMENT:** When the element is capable of delivering energy independently for long time (approximately infinite time). OR

• When the element is having property of internal amplification.

eg:- Voltage source (V), Current source (I), } Independent
 Transistor & op-amp. } Dependent


* Cap vs independent sources:

• During discharging capacitor can deliver the energy independently for short time^① and capacitor is not having internal amplification^② property.

PASSIVE ELEMENT:- when the element is not capable of delivering energy independently.

eg:- Resistor, bulb, transformer $(V_1 I_1 = V_2 I_2) \Rightarrow$ no internal amplification
 $P_{in} = P_{out}$

Ideal V source:

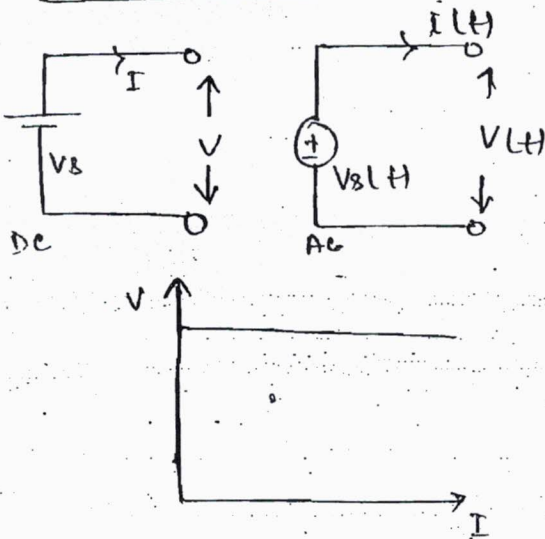

DC \rightarrow no time mentioned
 AC \rightarrow time mentioned


$R_s = 0$ $V = V_s$ $V \neq f(I)$

\rightarrow Ideal voltage source delivers energy at specified voltage (V) which is independent on current delivered by source.

\rightarrow Internal Resistance of ideal voltage source = 0.

Independent voltage source does not satisfy ohm's law since VI characteristics is not linear. (does not cross origin or not linearly?)

Practical V source:

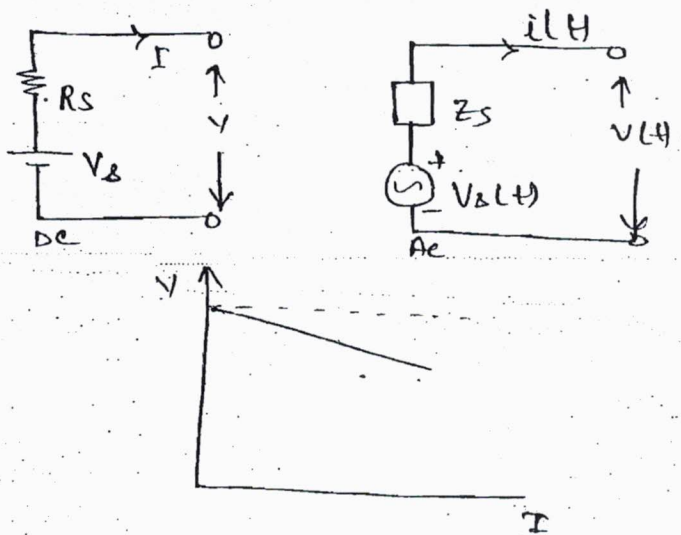

For DC: $V_s = V + I R_s$


$V = f(I)$ or $V = V_s - I R_s$ $V \downarrow$ as $I \uparrow$

\rightarrow Practical voltage source delivers energy at specified voltage (V) which depends on current delivered by the source.


\rightarrow Internal Resistance of practical voltage source = R_s

$R_s \neq 0$

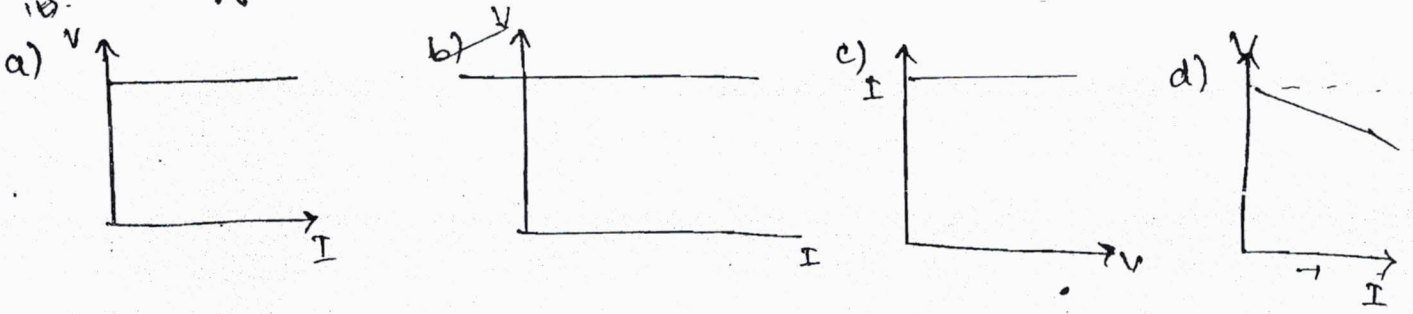
Q. Identify $V-I$ characteristics of ideal voltage source



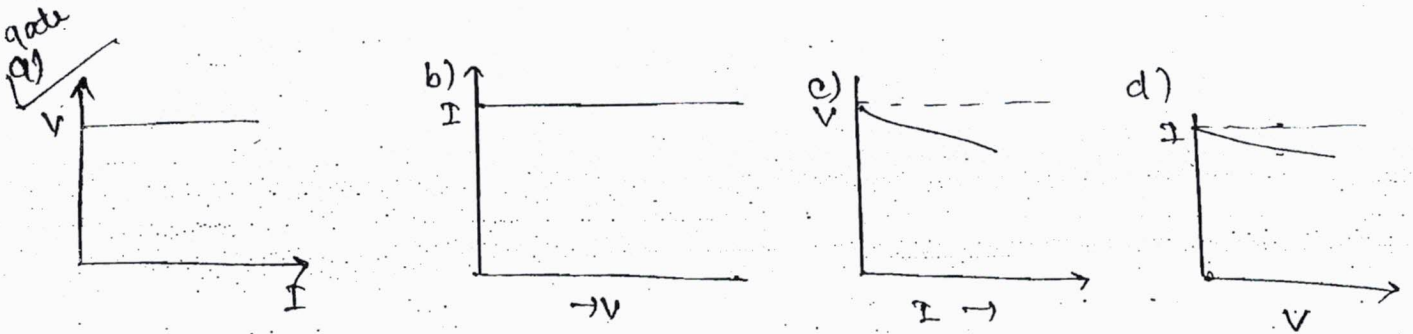Q. Same - Identify $V-I$ charact of ideal volt source.




∴ Considering a simple example:-






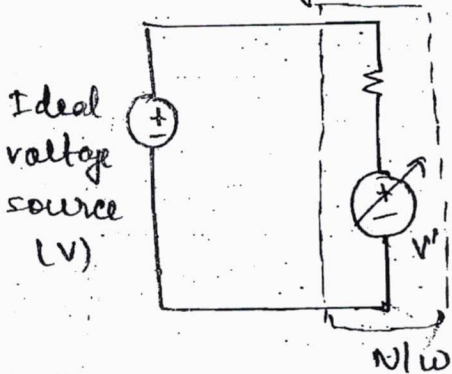


if $V' > V \Rightarrow I = (\text{clockwise})$
 $V' < V \Rightarrow I = (\text{anticlockwise})$
 $V' = V \Rightarrow I = 0$
 * * for both directions of I , V is constant, hence I consider in both +ve & -ve direction * *


If both options $Q_1(a, b) \rightarrow$ select b \rightarrow most appropriate
 one option $Q_2(a) \rightarrow$ select a.

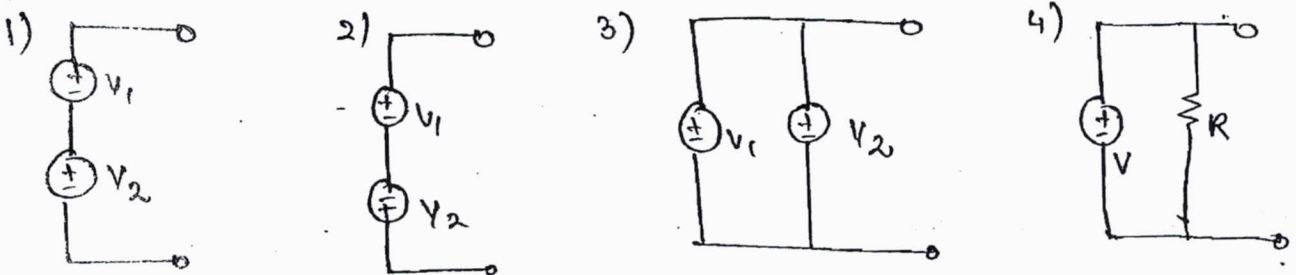Q. Find equivalent ct corresponding to them:-



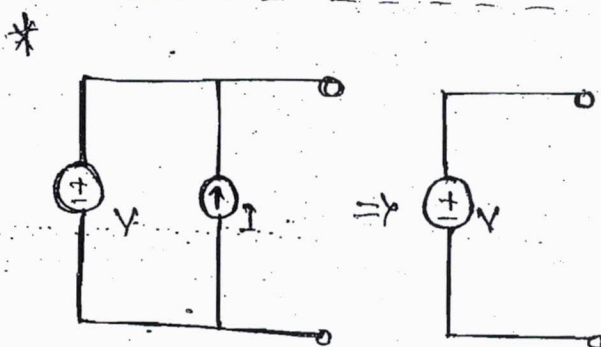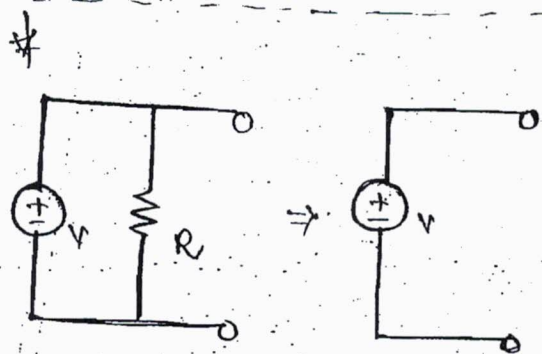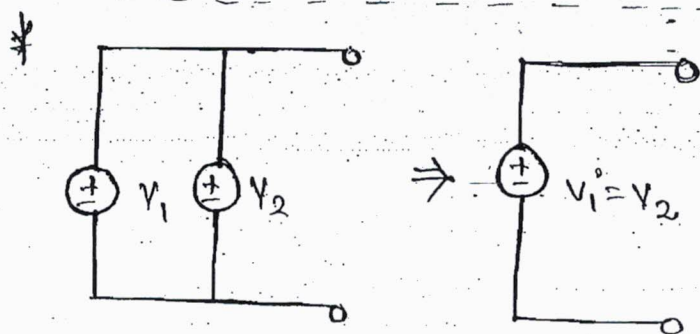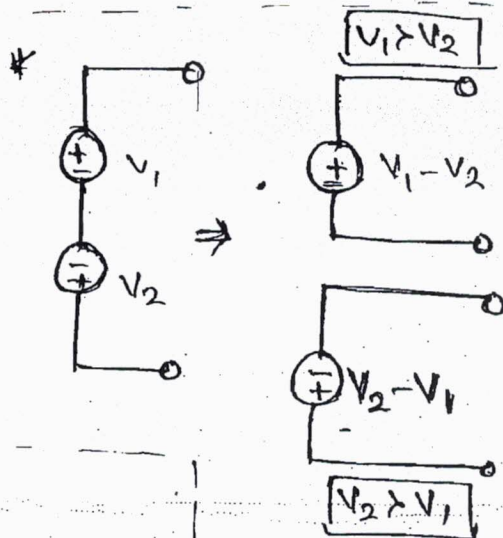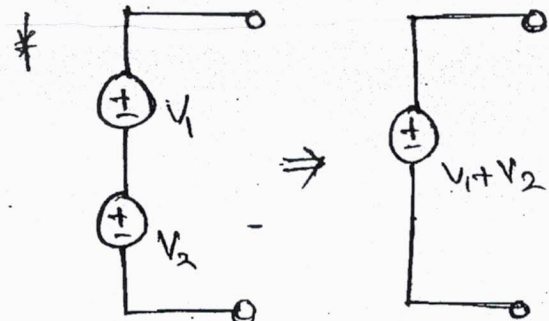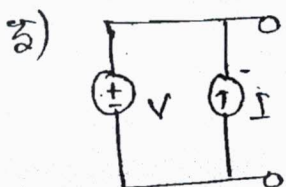


Q. Find current in the 2Ω resistance

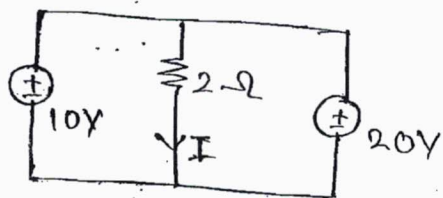

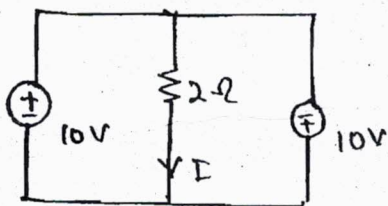- a) 5A b) 10A
 - c) 15A d) None or
- (NOT satisfying KVL) or
(0)

NOTE:-


With respect to KVL, voltage across all the parallel branches should be equal.




⇒ polarity as well as magnitude of voltages in parallel branches should be equal. Hence,

NOT satisfying KVL $\therefore I = 0$
 $10V \neq -10V$

Q.

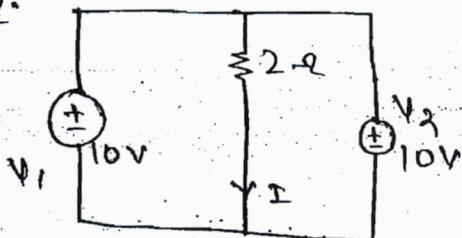


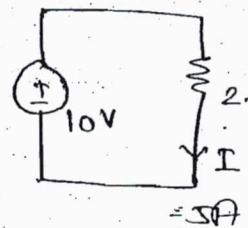$10V = IR$
 $\therefore I = \frac{10V}{2} = 5A$




• Verifying by using superposition theorem:-

Case 1 due to V_1 ;

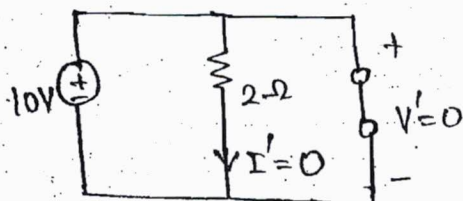

Case 2 due to V_2 .

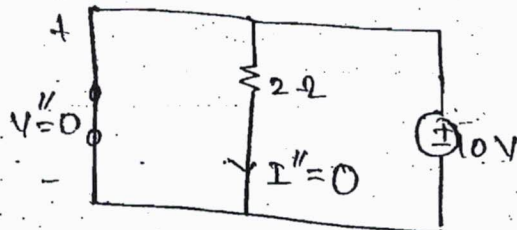

$I = I' + I'' = 0$


$10V + V' \neq \therefore$ KVL not satisfied

$10V + 10V \rightarrow$ not satisfying KVL

∴ The superposition does not apply.



NOTE:-

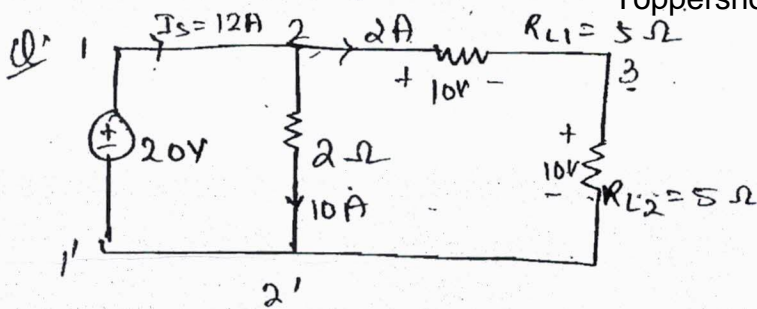For the above N/w superposition theorem cannot be applied since Case 1 + Case 2 circuits are not satisfying KVL.



$$V_{11'} = V_{22'} = V_{232'}$$

↓
parallel branches

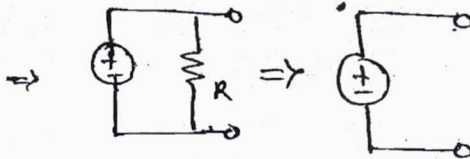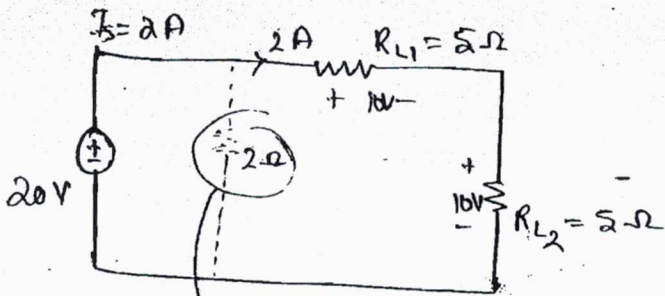

R not important/justifying ckt (4) from previous.

In 1st ckt; $P_s = 20 \times 12 = 240W$

In 2nd ckt; $P_s = 20 \times 2 = 40W$

→ not justifying ckt (4)


∴ Conclusion: → R can be neglected w.r.t load calculations (V_L, I_L)

R cannot be neglected w.r.t source current & source power


NOTE:- In above N/w, 2Ω resistance (10A current) can be neglected to calculate as a load current or load voltage.

However, in above N/w, 2Ω resistance (10A current) cannot be neglected to calculate either source current or source power.

Q. Find V_o on the n/w shown.

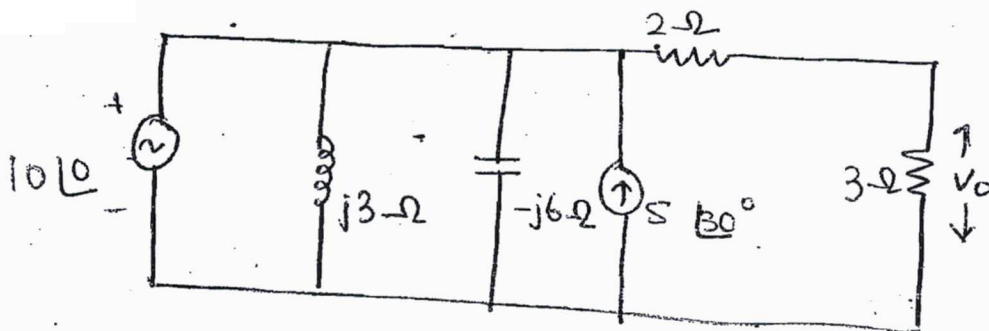

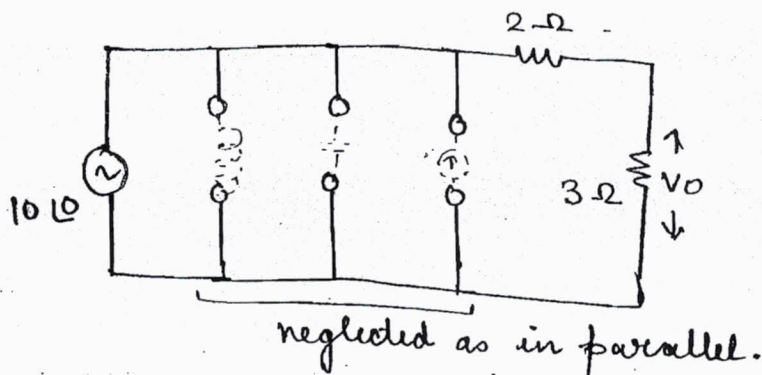⇒ Equivalent ckt for solving can be reduced to




$$I = \frac{10}{5} = 2 \text{ A}$$

$$V_0 = I \times 3 \Omega$$

$$V_0 = 6 \text{ V (ans)}$$

• Ideal Current Source -

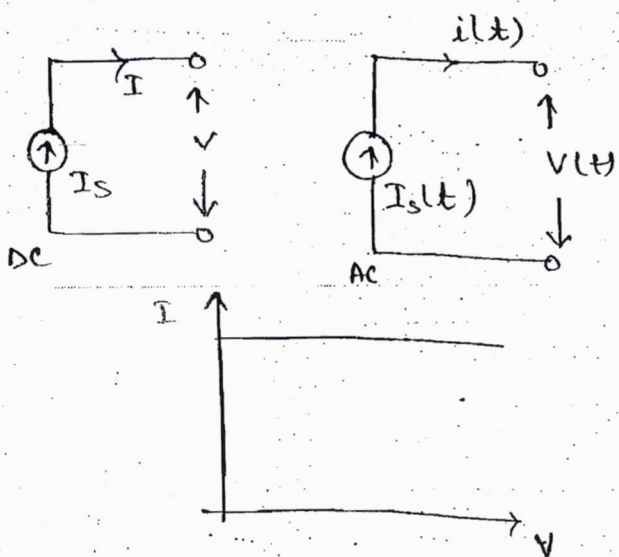


$$R_s = \infty$$

• Ideal current source delivers energy at specified current (I) which is independent of voltage across the source.

• Internal resistance of ideal current source = ∞

• Practical Current Source -

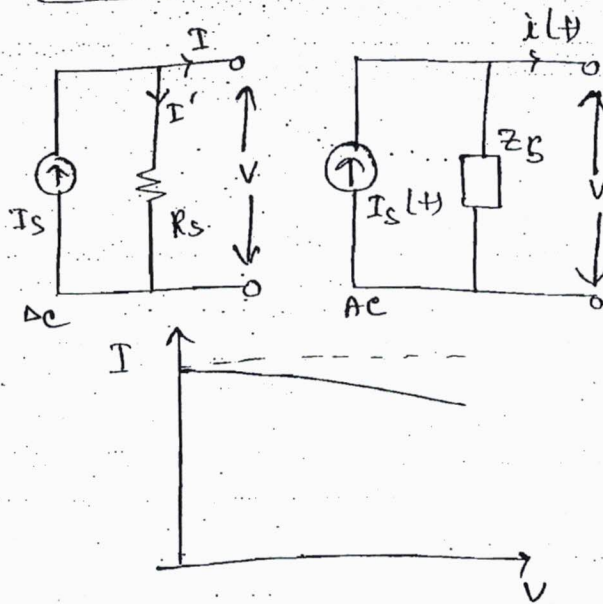

$$I_s = I' + I$$





$$\Rightarrow I = I_s - I' \text{ or } I = I_s - \frac{V}{R_s}$$

$$I \propto V$$

• Practical current source delivers energy at specified current (I) which depends on voltage across the source.


Conclusion: - Independent current source, does not obey Ohm's law, since VI characteristics is non-linear.

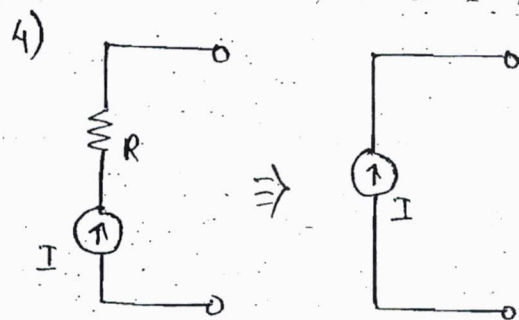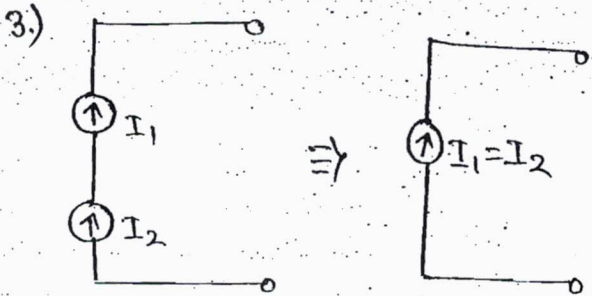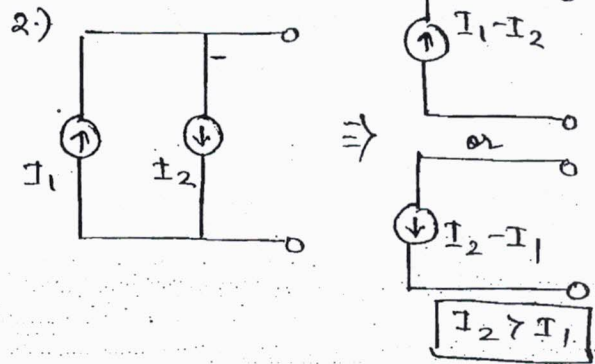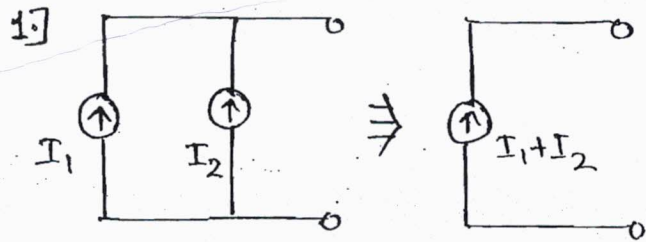- ✓ Internal resistance of ideal voltmeter = ∞
- ✓ " " " ideal ammeter = 0 $\rightarrow R_s$ (ideal)
- ✓ In the practical system independent current source does not exist but dependent current source exists.
eg:- Transistor \rightarrow theoretical concept for source transformation.




← Equivalent topologies for various NLS with ideal current source

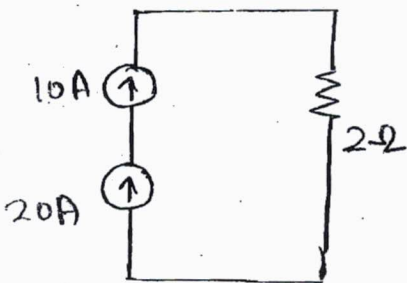Q Find equivalent current in 2Ω resistor.




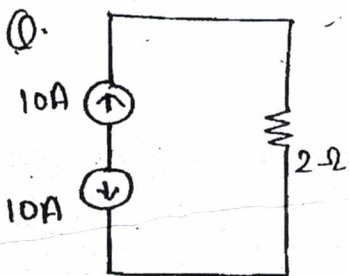- a) $10A$
- b) $20A$
- c) $30A$
- ✓ d) None or Not satisfying KCL

NOTE:- With respect to KCL, current flowing through all the series elements should be equal.







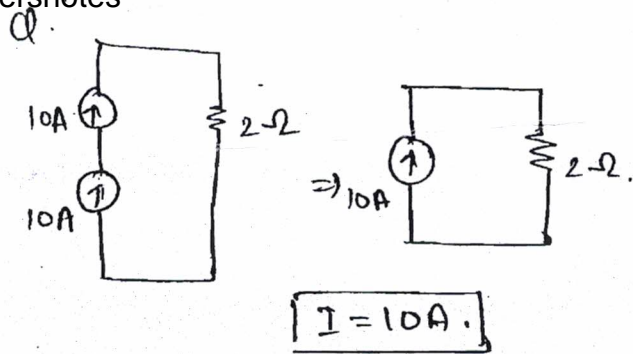not satisfying KCL at both direction + magnitude should be same.



$I = 10A$

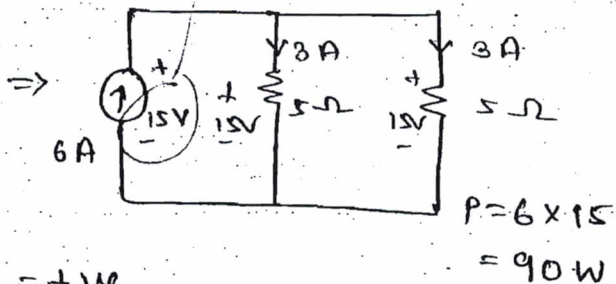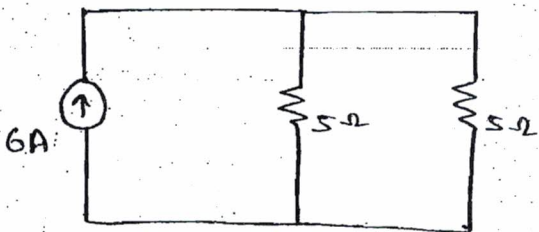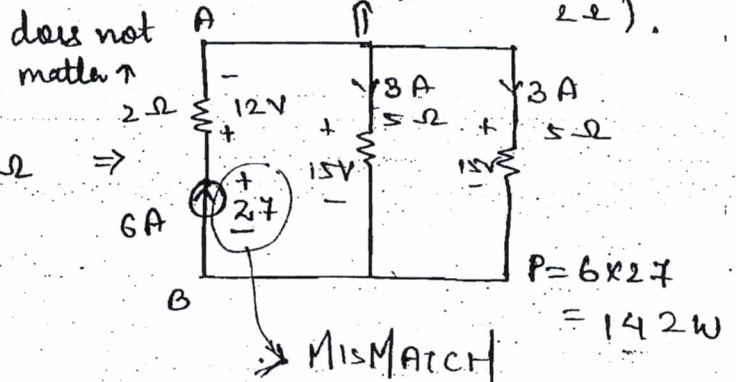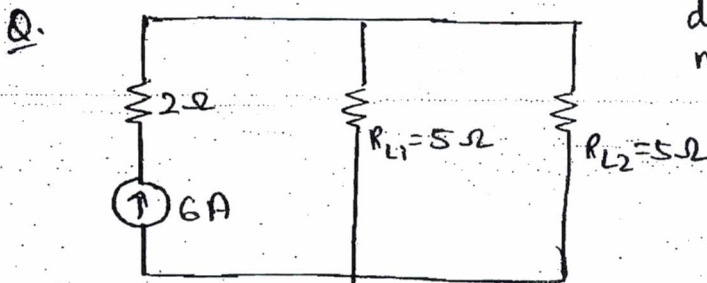Property (4) for load is verified (with without 2Ω).



Notations:- when current entering = +ve corresponding to arrow $\uparrow \pm$


$V_{AB} = V_S - 12 \Rightarrow 15 = V_S - 12 \Rightarrow V_S = 27$ ($V_S > 12$) \rightarrow Considered as source volt is greater.

NOTE:- In above N/W:-

2Ω resistance (12V voltage) can be neglected wrt load calculation $\parallel (V_L + I_L)$

but it cannot be neglected wrt source calculations [current, voltage or power of current source]


$\parallel (I_{IS}, V_{IS}, P_{IS})$

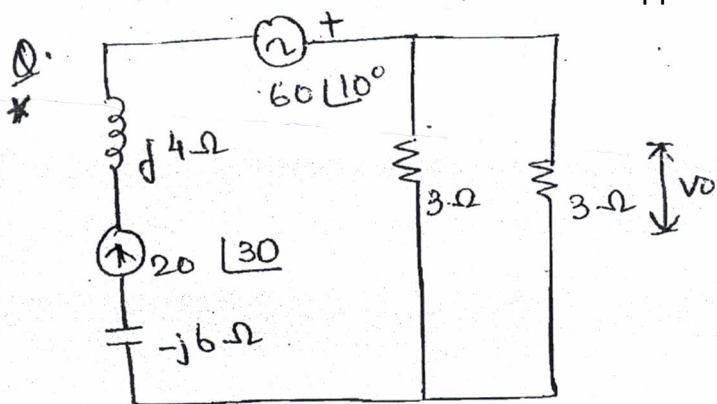

Find V_o .


* All elements in series to current source are neglected *

Equivalent ckt: \rightarrow


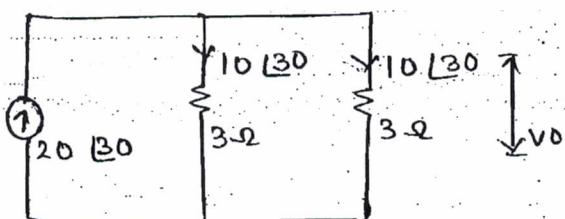


$\therefore V_o = 3 \times 10 \angle 30^\circ$


$V_o = 30 \angle 30^\circ \text{ V}$

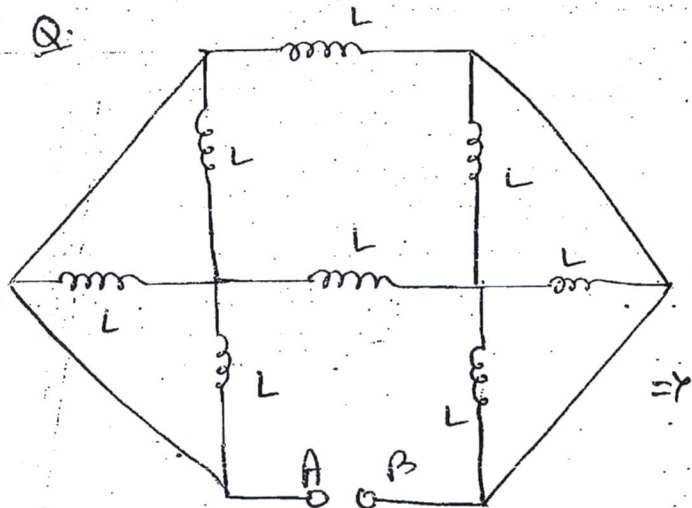

1) Find equivalent inductance with A+B.

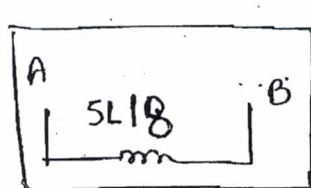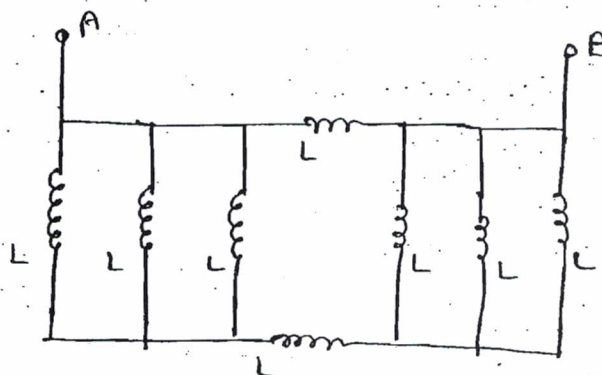


Req = $\frac{5L}{3} \parallel L$

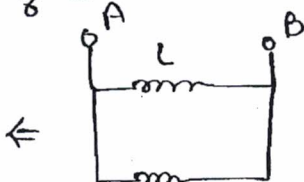

$\frac{5L}{3}$


$\leftarrow \frac{L}{3}$

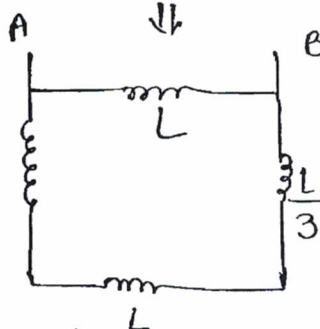


$L \parallel \frac{5L}{3}$

$\Rightarrow \frac{L \times \frac{5L}{3}}{L + \frac{5L}{3}} = \frac{L^2 \cdot \frac{5}{3}}{4L} \left(\frac{L}{3} + L + \frac{L}{3} \right)$

Series & Parallel Connection


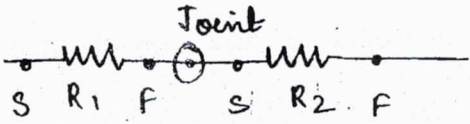


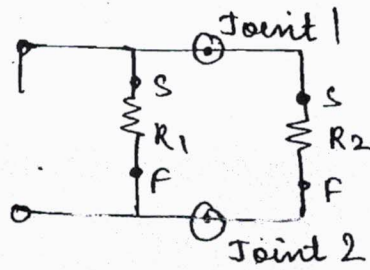- 1) One joint (F-S)
- 2) Same current (I) flows through both





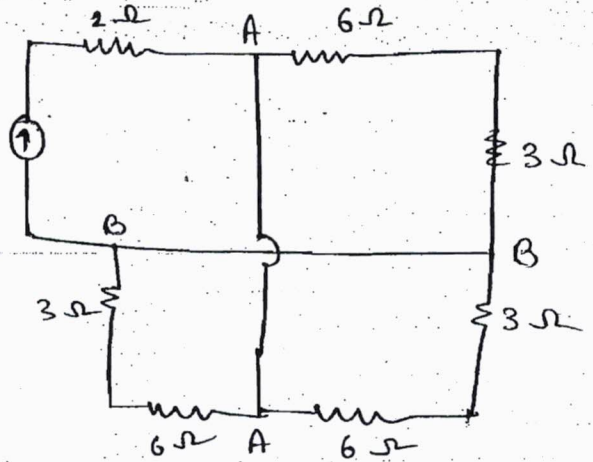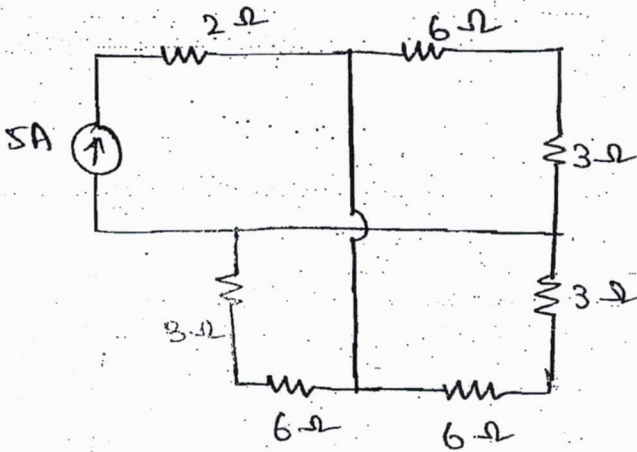- 1) Two joints (S-S)
- 2) Same voltage through both

Q. Find power delivered by current source.



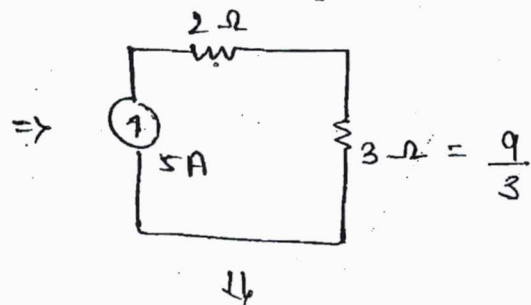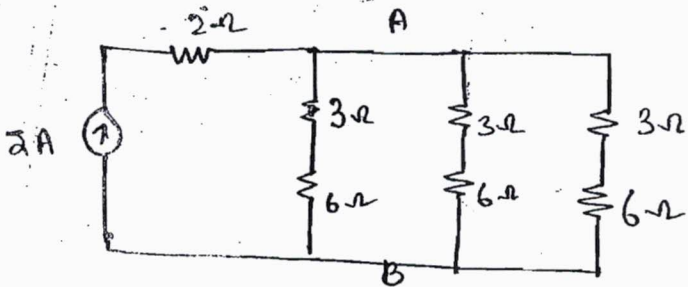⇒ A to B + 3 branches ∴ all branches in parallel.



$$\begin{aligned}
 \text{Power} &= I^2 R \\
 &= 25 \times 5 \\
 \boxed{P} &= \boxed{125 \text{ W}}
 \end{aligned}$$

