

IES / GATE

Electrical Engineering

VOLUME-VII

Electrical Machines


CONTENT

A. Ideal Transformer	5
1. Open circuit test or Short circuit test	16
2. Transformer Parameters	18
3. Voltage Regulation	26
4. Losses in Transformer	35
5. Auto Transformer	39
6. Parallel Operation of Transformer	81
7. Magnetizing Current Phenomena	95
B. DC Machines	109
1. Armature Reaction	127
2. Generator	142
3. Braking	168
4. Ward leonard System	178
C. Synchronous M/C	187
1. Synchronous Generator	190
2. Armature Reaction	201
3. Voltage Regulation of Alternators	216
4. Synchronization	246
5. Salient Pole Synchronous Machine	263
D. 3-ϕ Induction Machine	276
E. Deep-bar Rotor & / Double-cage Rotor	315
F. CRAWLING	327
G. 1-ϕ Induction Motor	331

Electrical Machines

Capable of Continuous Electromechanical Conversion is called Electrical machines.

Transformers

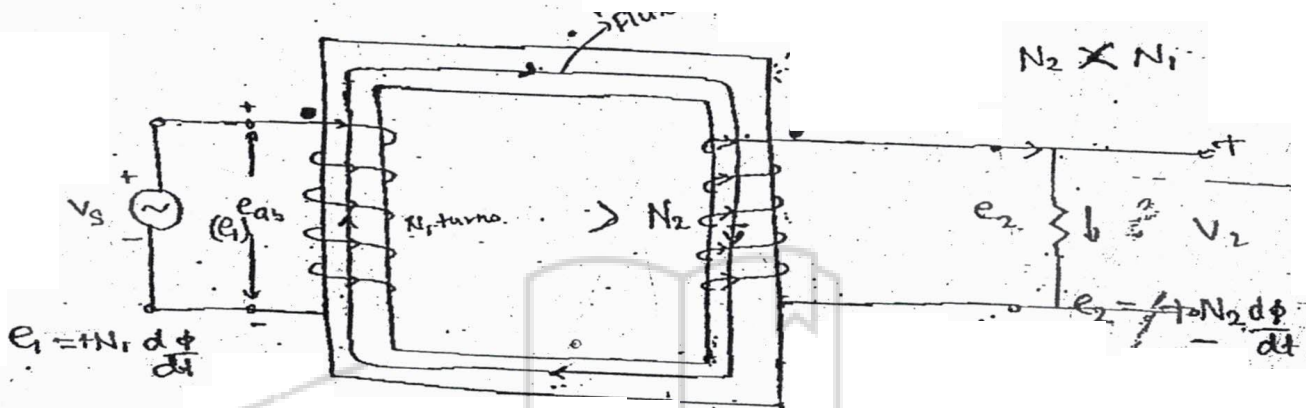

Core: - Provide low reluctance magnetic path


* According to Lenz's law, the direction of induced emf is such that if it is allowed to cause a current by short circuiting the coil then the current so produced opposes the causes.

Thus,
$$e = \pm \frac{d\lambda}{dt}$$


$$e_{ab} = + N_1 \frac{d\phi}{dt}$$

when $\lambda = \text{flux linkage} = N\phi$.

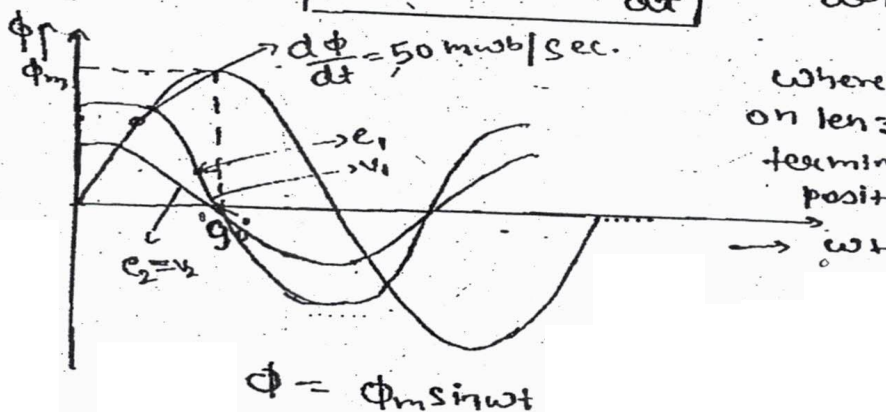where the sign depends on Lenz's law and which terminal is taken as positive.




welsan daitero

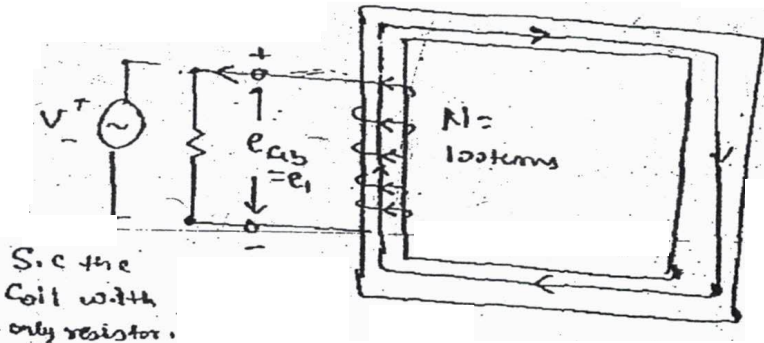

S.c the coil with only resistor.
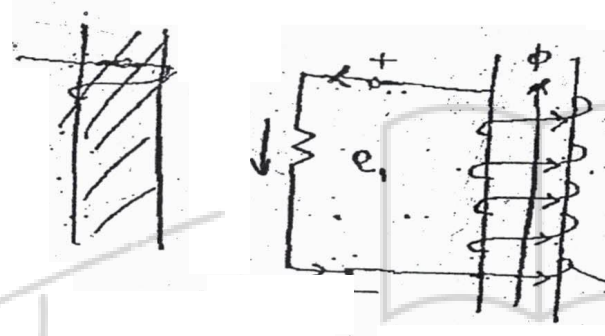
$$\begin{aligned}
 e_1 = e_{as} &= N_1 \frac{d\phi}{dt} \\
 &= 100 \times 50 \times 10^{-3} \\
 &= 5 \text{ volt}
 \end{aligned}$$



$$\begin{aligned}
 e_1 &= -N_1 \frac{d\phi}{dt} \\
 &= -100 \times 50 \times 10^{-3} \\
 &= -5 \text{ v}
 \end{aligned}$$


Sense of ω changes

$$\begin{aligned}
 e_1 &= N_1 \frac{d\phi}{dt} \\
 &= N_1 \frac{d(\phi_m \sin \omega t)}{dt} \\
 &= N_1 \phi_m \omega \cos \omega t \\
 &= N_1 \phi_m \omega \sin(\omega t + 90^\circ)
 \end{aligned}$$

$$E_1 = \frac{N_1 \phi_m \omega}{\sqrt{2}}$$

$E_1 = \sqrt{2} \pi f \phi_m N_1$

Induced Emf equation

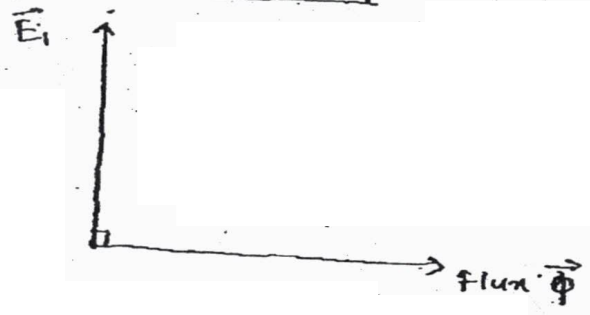


Concept of phasors

$$\sum V = 0$$

$$-e_1 + v_1 = 0$$

$$\Rightarrow v_1 = e_1$$

$$\Rightarrow \vec{E}_1 = \vec{V}_1$$

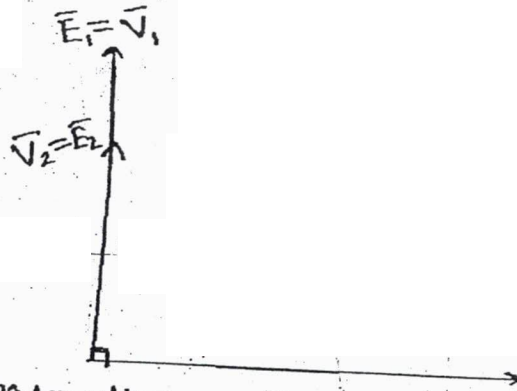

Phasor diagram of ideal transformer on no-load

Vector has a fixed magnitude & fixed direction.

But Sinusoids are the phasors not the vectors.

Phasor diagrams only shows phase relation.

$\vec{E}_1 = \vec{V}_1$ it does not mean

V_1 supports E_1

but in vector,

\vec{A} (Concept of vector)

$\vec{A} + \vec{B} = 0$ (They are opposing)


but in phasor, it is not determined.

Concept of phasor

→ A phasor diagram has no meaning without ckt diagram and vice-versa.


→ Phasor diagram only show that both \vec{E} & \vec{V} are rising together or decaying together and lag & lead and nothing else.

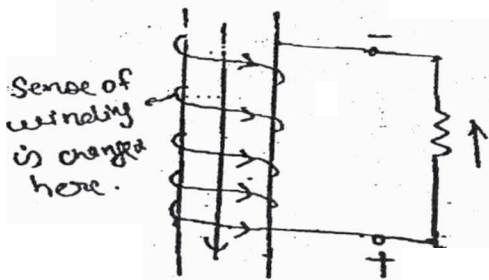→ They are supporting and opposing each other is determined by circuit diagram.



Dot Convention

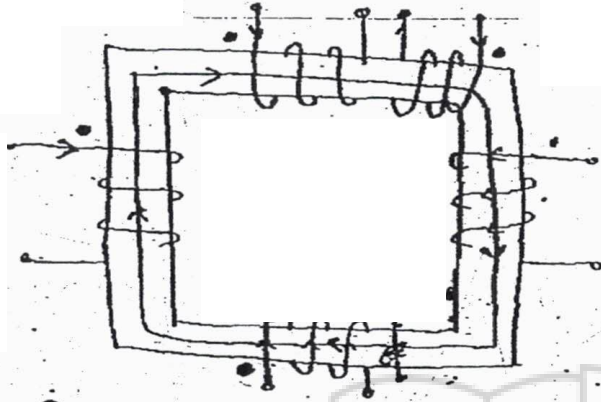If the current enters or leaves through the dot simultaneously, then the fluxes are additive.



Only the first dot is assigned. The remaining dots follow automatically depending upon the sense of winding.

As applied to a transformer, therefore if the current enters through the dot in one winding then it should leave through the dot from the other winding to satisfy Lenz law. In other words the dots have the same instantaneous polarity.

$$\begin{aligned}
 e_2 &= +N_2 \frac{d}{dt} (\Phi_m \sin \omega t) \\
 &= +N_2 \Phi_m \omega \cos \omega t \\
 &= N_2 \Phi_m \omega \sin(\omega t + 90^\circ)
 \end{aligned}$$

$$\Rightarrow E_2 = \frac{N_2 \Phi_m \omega}{\sqrt{2}}$$

$$E_2 = \sqrt{2} \pi f \Phi_m N_2$$

Ideal transformer

- 1) No losses
- 2) Infinite permeability

$$\Phi = \frac{NI}{S \text{ -reluctance}}$$

$$\Rightarrow NI = \Phi S = \Phi \frac{l}{\mu_0 \mu_r} \Rightarrow NI = \Phi \times \frac{l}{\mu_0 \mu_r}$$

- No winding losses
 - No core losses
 - No exciting current required
 - Zero magnetizing current.
- $= 0$ though $\Phi \neq 0$

Property of a magnetic ckt.

If any magnetic ckt. is applied with an alternating excitation then it must produce an emf. which is equal and opposite in nature.

MMF balance of ideal X-former:

$$N_1 \bar{I}_1 + N_2 \bar{I}_2 = 0$$

$$N_1 \bar{I}_1 = -N_2 \bar{I}_2$$

$$\Rightarrow \bar{I}_1 = \frac{N_2}{N_1} \times \bar{I}_2 = \frac{I_2}{a} = \bar{I}_2'$$


Primary current referred to secondary

$$\frac{V_1}{V_2} = \frac{E_2}{E_1} = \frac{N_1}{N_2} = a = \frac{I_2}{I_1} = \frac{I_2^*}{I_1^*}$$

↓
Turns ratio
or
Voltage ratio


$$\left. \begin{aligned} \Rightarrow \vec{V}_1 \vec{I}_1^* &= \vec{V}_2 \vec{I}_2^* \\ \& \vec{E}_1 \vec{I}_1^* &= \vec{E}_2 \vec{I}_2^* \end{aligned} \right\} \Rightarrow \bar{S}_1 = \bar{S}_2$$

Conduct ~~near~~
~~device~~

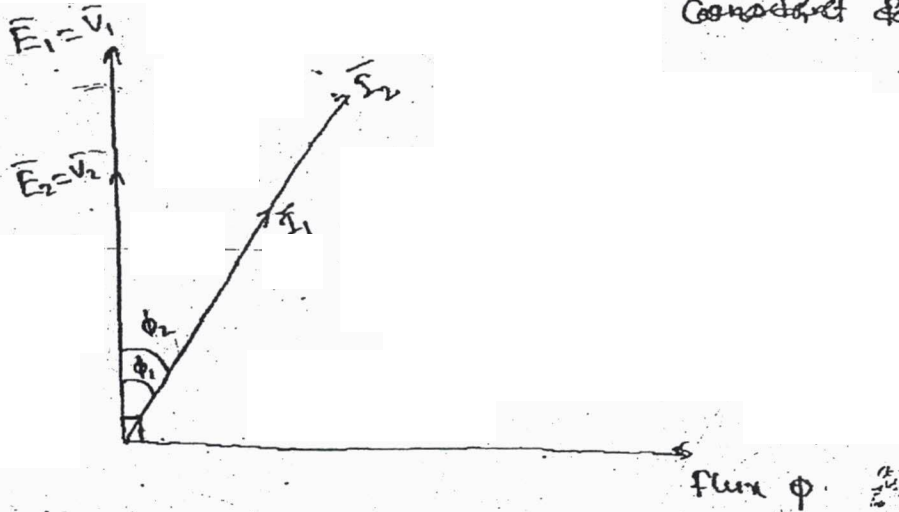


Magnetizing current \rightarrow 2 to 3%

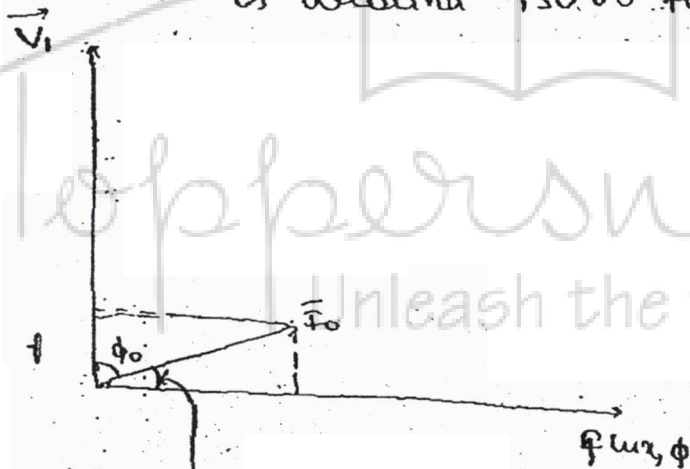
because we do not have any intentional gap we have a iron core whose permeability is around 150,00 to 20,000



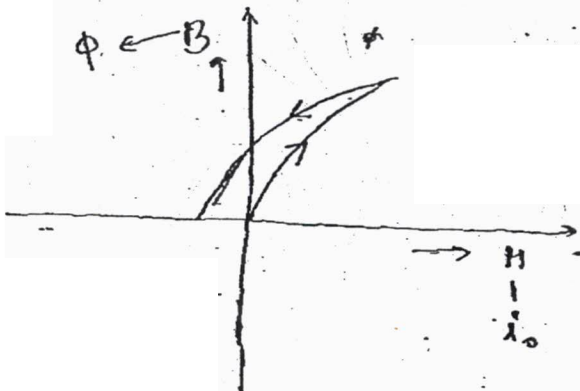Angle of Hysteretic Advance or Hysteretic lag angle } decided by position of observer



is lead or when observer seen from ϕ .

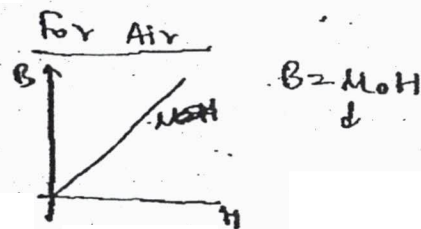

MMF Balance of Practical transformer

$$\vec{N}_1 \vec{I}_1 = \vec{N}_2 \vec{I}_2 = N_1 \vec{I}_0$$

$$\vec{N}_1 \vec{I}_1 = N_2 \vec{I}_2 + N_1 \vec{I}_0$$

$$\Rightarrow N_1 \vec{I}_1 = N_2 \vec{I}_2 + N_1 \vec{I}_0$$

$$\vec{I}_1 = \frac{N_2}{N_1} \times \vec{I}_2 + \vec{I}_0$$


$$= \frac{I_2}{a} + \vec{I}_0 \Rightarrow I_2' + \vec{I}_0$$

$I_0 \rightarrow$ No load current / Exciting current.

$I_0 \rightarrow$ magnetizing current if it is ideal transformer

$I_\phi =$ magnetizing current

$I_c =$ core loss component

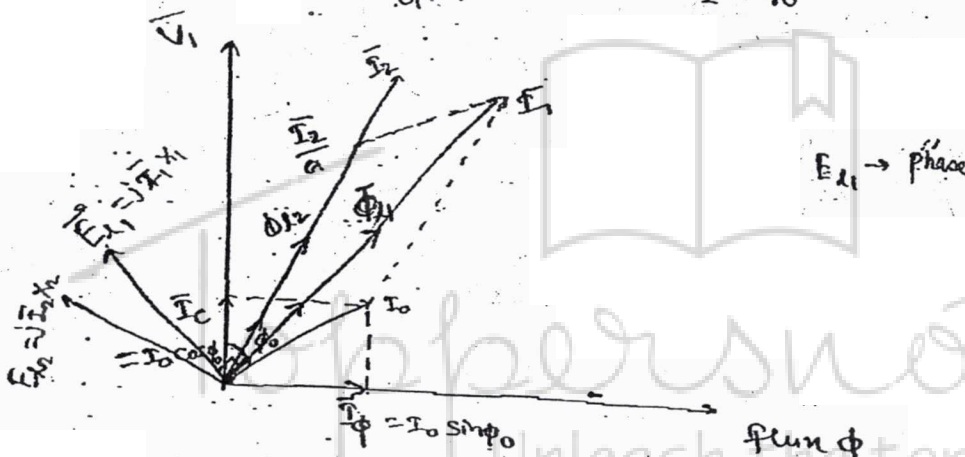


$\phi_0 =$ no load pf load (around 80°)

$R_1 =$ Primary winding resistance }
 $R_2 =$ Secondary winding resistance } (Shown outside the winding in diagram)

$\phi_{lm} =$ leakage flux in magnetic ckt.

Electric ckt. \rightarrow Electric current confined by the insulation & not deviate from its path, if there is a leakage that will be very minute.

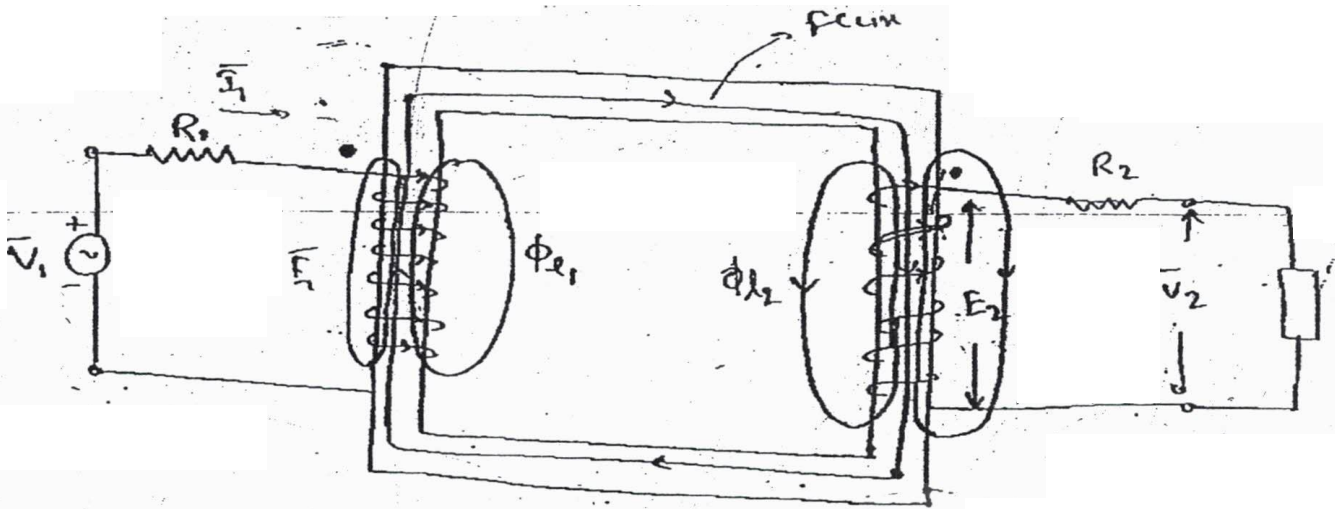Magnetic ckt. \rightarrow Magnetic flux will made itself in the free space or air. Also there is leakage that is considerable.




→ Φ_{e1} is in phase with I_1

$$B = \mu_0 \mu_r H$$

↓
Permeability of core

→ Mutual flux is responsible for transfer of power in any electrical machine

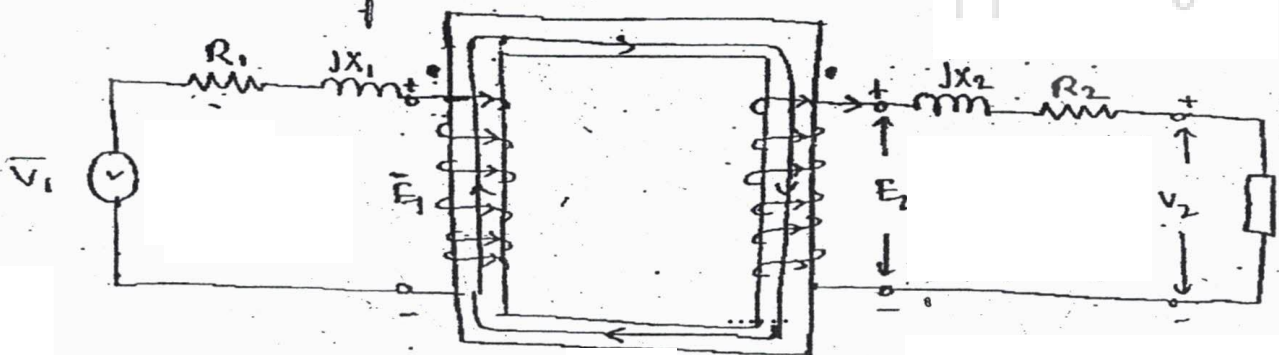→ Leakage flux is only a choke in series which only drops voltage



$$1) \quad \bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + j \bar{I}_2 X_2$$

$$\Rightarrow \bar{E}_2 = \bar{V}_2 + \bar{I}_2 (R_2 + jX_2)$$

$$\Rightarrow \bar{E}_2 = \bar{V}_2 + \bar{I}_2 \bar{Z}_2$$

$$2) \quad \bar{E}_1 = a \bar{E}_2$$

$Z_2 =$ Secondary leakage impedance

3)
$$\vec{I}_1 = \frac{\vec{I}_2}{a} + \vec{I}_0$$

$$= \vec{I}_2' + \vec{I}_0$$

where $\vec{I}_0 = \vec{I}_E + \vec{I}_\phi$


\downarrow phase with E_1
 \downarrow phase with \vec{I}_2 in

4)
$$\vec{V}_1 = \vec{E}_1 + \vec{I}_1 R_1 + j \vec{I}_1 X_1$$


$$= \vec{E}_1 + \vec{I}_1 (R_1 + j X_1)$$

$$V_1 = \vec{E}_1 + \vec{I}_1 \vec{Z}_1$$

||| → Shows tight coupling

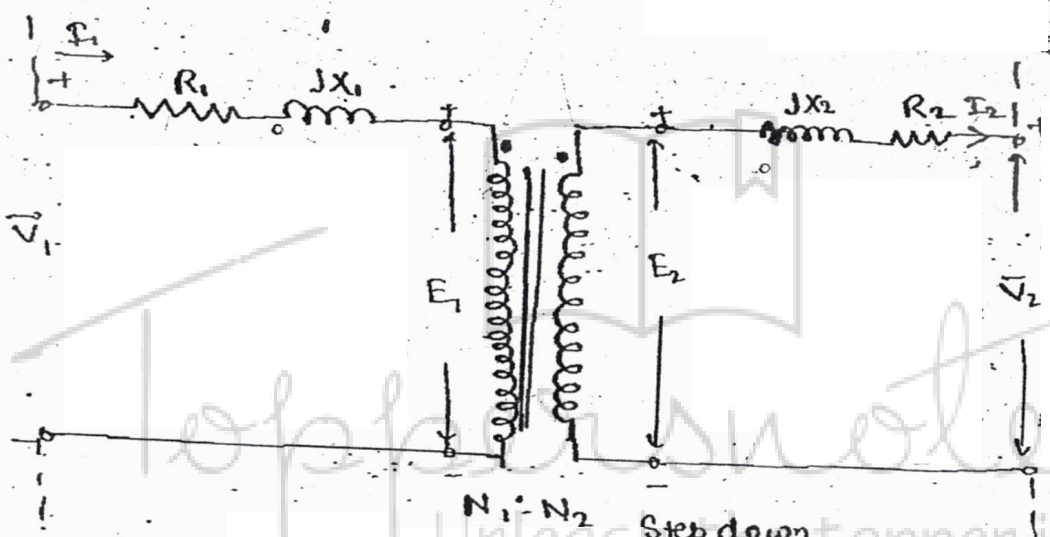

Lagging PF:

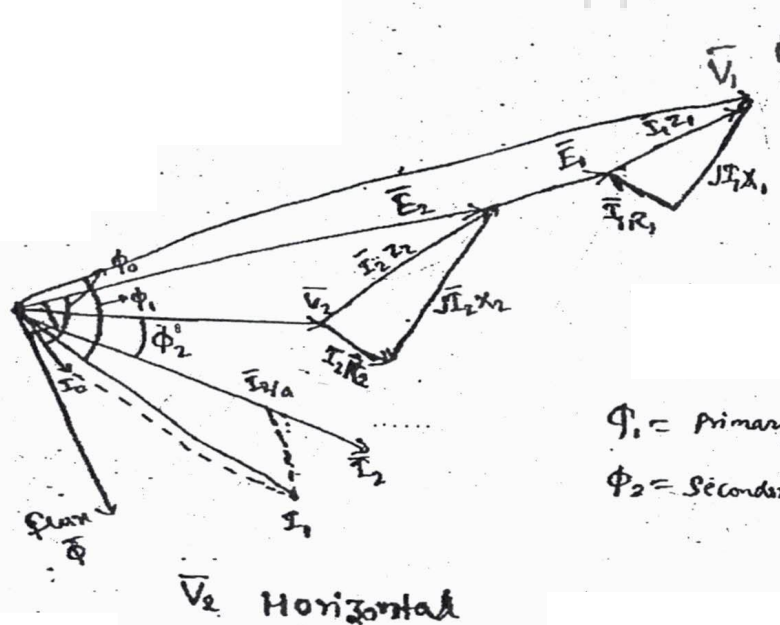

$\phi_1 =$ Primary PF Angle
 $\phi_2 =$ Secondary PF Angle


\vec{V}_2 Horizontal

flux horizontal

$$\bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + j \bar{I}_2 X_2$$


$$\bar{V}_2 = \bar{E}_2 - \bar{I}_2 R_2 - j \bar{I}_2 X_2$$

known to unknown

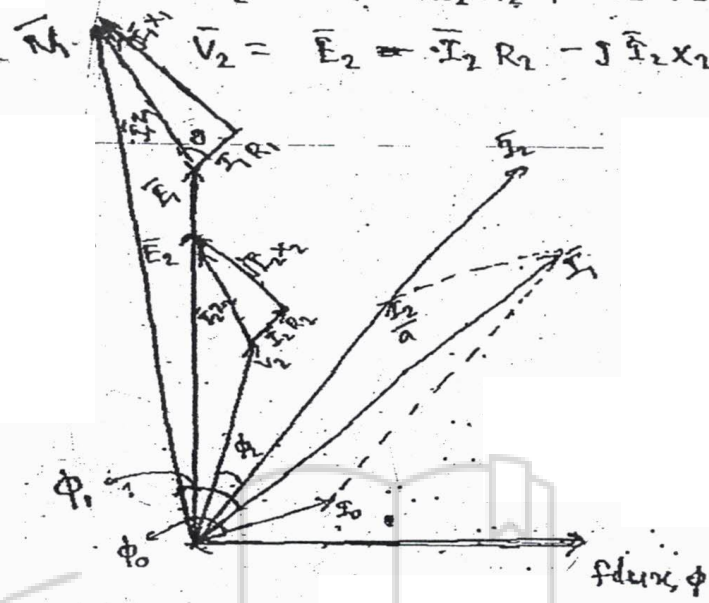

~~Leading PF~~
Leading PF

V₂ horizontal

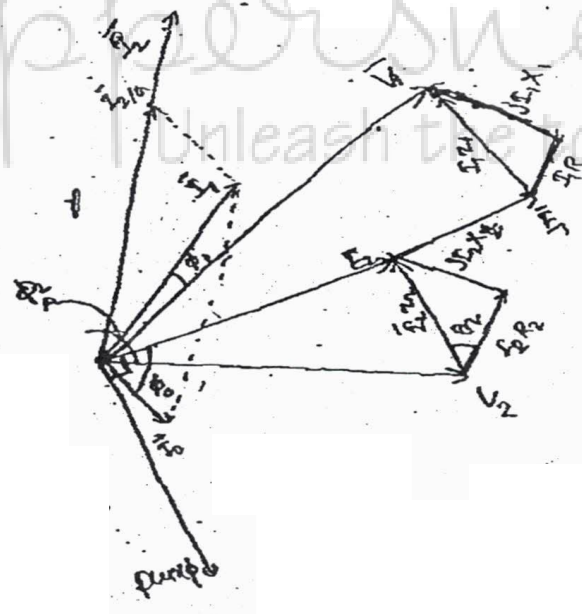

Equivalent Ckt. of Transformer

* Representation of any device by standard active, & passive ckt. elements that can be used to analyse and predict the performance of the device is its equivalent ckt.

$$\vec{E}_2 = \vec{V}_2 + \vec{I}_2 R_2 + j \vec{I}_2 X_2$$

multiplying by $\frac{N_1}{N_2} = a$

$$\Rightarrow a \vec{E}_2 = a \vec{V}_2 + a \vec{I}_2 R_2 + j a \vec{I}_2 X_2$$

$$\Rightarrow \vec{E}_1 = \vec{E}'_2 = \vec{V}'_2 + \left(\frac{\vec{I}_2}{a}\right) (a^2 R_2) + j \left(\frac{\vec{I}_2}{a}\right) (a^2 X_2)$$


$$= \vec{V}'_2 + \vec{I}'_2 R'_2 + j \vec{I}'_2 X'_2$$

\downarrow
 Secondary resistance referred to primary

\downarrow
 Secondary leakage reactance referred to primary

$$= \vec{V}'_2 + \vec{I}'_2 (R'_2 + j X'_2)$$
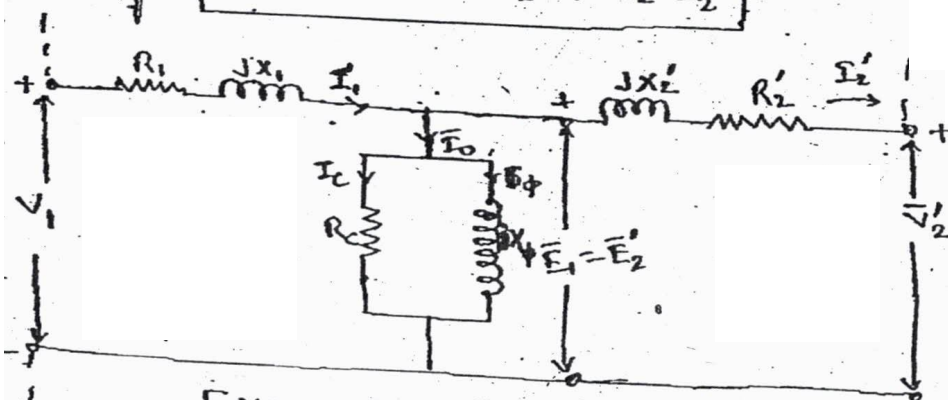
$$\Rightarrow \vec{E}_1 = \vec{E}'_2 = \vec{V}'_2 + \vec{I}'_2 \vec{Z}'_2$$



Exact Equivalent Ckt. referred to primary

R_c = core loss equivalent resistance

X_ϕ = magnetizing reactance

Because of shape of ckt., it is known as (T-equivalent)

X_ϕ & R_c is || Element as it is dependent on Applied Voltage.

Secondary Side Parameters when Referred to Primary.

$$R_2' = a^2 R_2 \quad \text{or} \quad \frac{R_2}{k^2} \quad \left\{ \begin{array}{l} \text{when } a = \frac{N_1}{N_2} \\ \text{or } k = \frac{N_2}{N_1} \end{array} \right\}$$

$$X_2' = a^2 X_2 \quad \text{or} \quad \frac{X_2}{k^2}$$

$$\left. \begin{array}{l} R_{01} = R_1 + R_2' \\ X_{02} = X_2 + k^2 X_1 \\ \quad = X_2 + X_1' \end{array} \right\} \quad X_{01} = X_1 + X_2'$$

$$I_2' = \frac{I_2}{a} \quad \text{or} \quad k I_2$$

$$E_2' = a E_2 \quad \text{or} \quad \frac{E_2}{k} \quad \& \quad V_2' = a V_2 \quad \text{or} \quad \frac{V_2}{k}$$

Pu reactance drop referred to 1° = $\frac{I_1 X_{01}}{E_1}$

" " " " " 2° = $\frac{I_2 X_{02}}{E_2}$


★ Pu reactance drop on both sides of TF is same

$$\frac{I_1 X_{01}}{E_1} = \frac{I_2 X_{02}}{E_2}$$

$$\% X = \frac{I_1 X_{01}}{E_1} \times 100 \quad \text{or} \quad \frac{I_2 X_{02}}{E_2} \times 100$$

250 kVA, 2500/250V
 ↓ = 1000A ← → 1000A
 (delivered o/p power) o/p terminal voltage

2500V / 250V
 ↓ ↓
 aV₂ / V₂

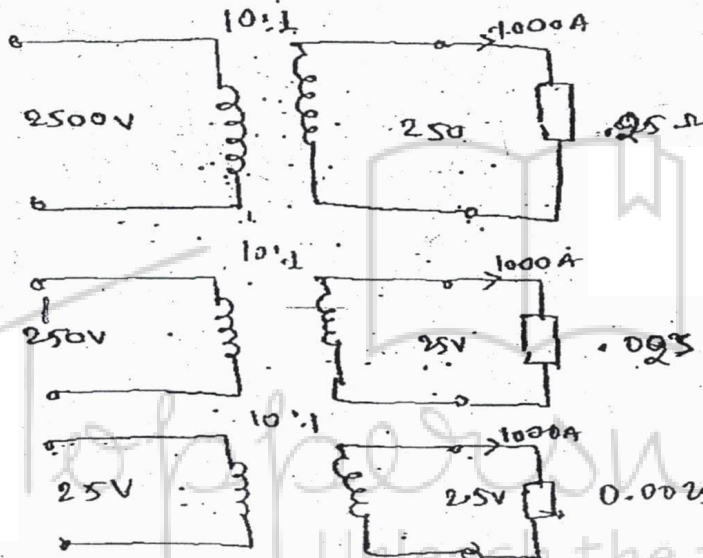

full load

full load current but not full load

2° referred to 1°
 $E_1 = a E_2 = E_2'$
 $I_2' = \frac{I_2}{a}$
 $R_2' = a^2 R_2$

1° referred to 2°
 $E_1' = E_2/a$
 $I_1' = a I_1$
 $R_1' = R_1/a^2$

$\frac{1000}{2500} = \frac{1000}{250}$
 $\frac{1000}{2500} = \frac{1000}{250}$

Full load \rightarrow Full load current is delivered at rated voltage.


Q. The parameters of Equivalent ckt. of 150 kVA, 2400V/240V transformer are. $R_1 = 0.2 \Omega$ $R_2 = 2 m\Omega$

$X_1 = 0.45 \Omega$ $X_2 = 4.5 m\Omega$

$R_c = 10 k\Omega$ $X_\phi = 1.55 k\Omega$

using the ckt. referred to primary determine primary i/p voltage, i/p current & input pf of x-former operating at rated load with 0.8 lagging pf

Q.

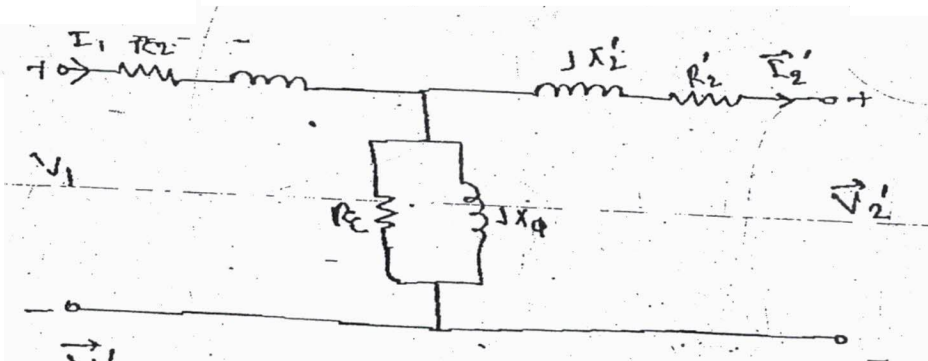

$$\begin{aligned} \vec{V}_2' &= a V_2 \angle 0^\circ \\ &= 10 \times 240 \angle 0^\circ \\ &= 2400 \angle 0^\circ \text{ Volts.} \end{aligned}$$

$$\begin{aligned} \vec{I}_2 &= \frac{150 \times 10^3}{240} \sqrt{1 - \cos^2(0.8)} \\ &= 625 \angle -36.87^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \vec{I}_2' &= \frac{\vec{I}_2}{a} = \frac{625}{10} \angle -36.87^\circ \text{ A} \\ &= 62.5 \angle -36.87^\circ \end{aligned}$$

$$\begin{aligned} \vec{Z}_2' &= a^2 \vec{Z}_2 \\ &= (10)^2 [(2 + j4.5) \times 10^{-3}] \\ &= (0.2 + j0.45) \Omega \end{aligned}$$

$$\begin{aligned} \vec{E}_1 &= 2400 \angle 0^\circ + 62.5 \angle -36.87^\circ \times (0.2 + j0.45) \\ &= 2426.92 \angle 0.35^\circ \text{ Volts} \end{aligned}$$


$$\vec{I}_c = \frac{\vec{E}_1}{R_c} = \frac{2426.92 \angle 0.35^\circ}{10 \text{ k}\Omega} = 0.2427 \angle 0.35^\circ \text{ A}$$

$$\vec{I}_\phi = \frac{\vec{E}_1}{jX_\phi} = \frac{2426.92 \angle 0.35^\circ}{1.55 \angle 90^\circ \text{ k}\Omega} = 1.5658 \angle -89.65^\circ$$

$$\begin{aligned} \vec{I}_0 &= \vec{I}_c + \vec{I}_\phi \\ &= 0.2427 \angle 0.35^\circ + 1.5658 \angle -89.65^\circ \\ &= 1.5845 \angle -80.84^\circ \end{aligned}$$

Kingley → Harvard. program

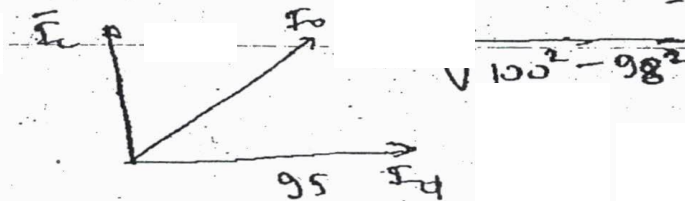$I_C = 98\% \text{ of } I_0$
 then what is $I_C = ?$ $I_C = \sqrt{100^2 - 98^2}$
 $= 15\%$



$$\vec{I}_1 = \vec{I}_2' + \vec{I}_0$$


$$= 63.65 \angle -37.86^\circ \text{ A}$$

$$\vec{V}_1 = \vec{E}_1 + \vec{I}_1 \vec{Z}_1$$

$$= 2426.92 \angle 0.35^\circ + 63.65 \angle -37.86^\circ \times (0.2 + j0.45)$$

$$= 2454.68 \angle +0.69^\circ$$

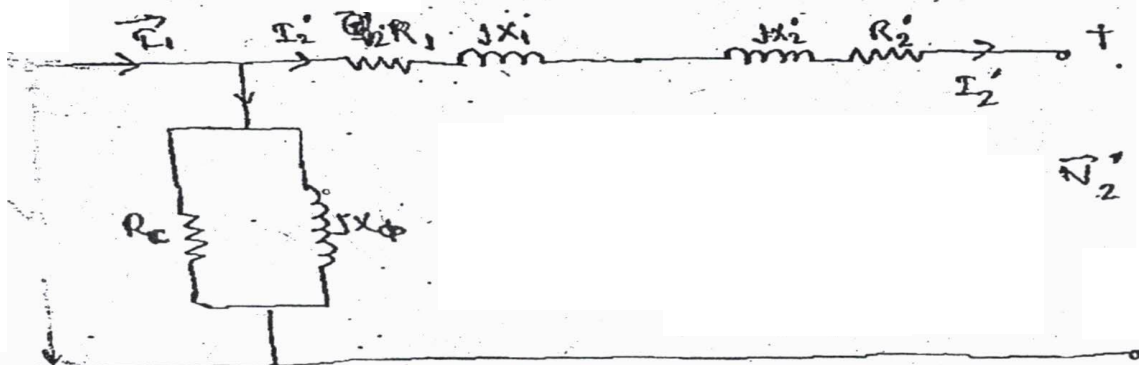Input PF = $\cos [0.69^\circ - (-37.86^\circ)]$
 $= \cos 38.55^\circ \text{ lag.}$
 $= 0.7821 \text{ lag//}$



(Just like Cantilever ckt) - 1st Approx. ckt.

Through magnetic ckt. we can transfer energy very efficient because magnetic flux density is 25000 times that of electric field density.